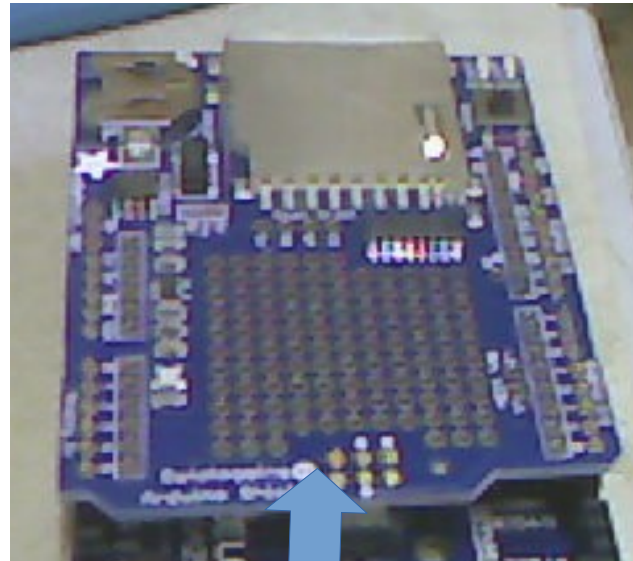


Chest Build Procedure

Names of Boards refer to this page to get the names of the components.





Mega 2560 (the brain)



Adafruit Data Logging
Shield (SD card board)

IMU (inertial
measurement Unit)

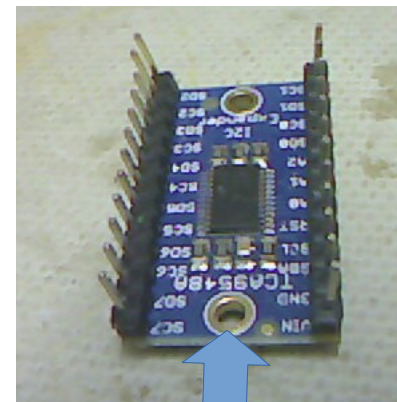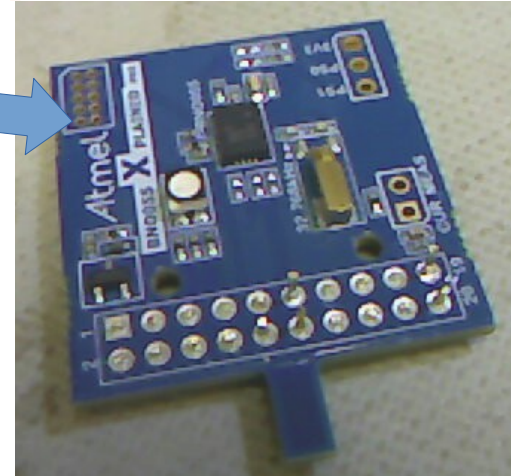


Adafruit I2C multiplexer
board.


During build make sure all solder joints connect the pin to the hole (no gold rings showing). Hold the iron for a second or two on the pin to let the solder wick into the shaft with the pin in it)



Print Out Chest Base

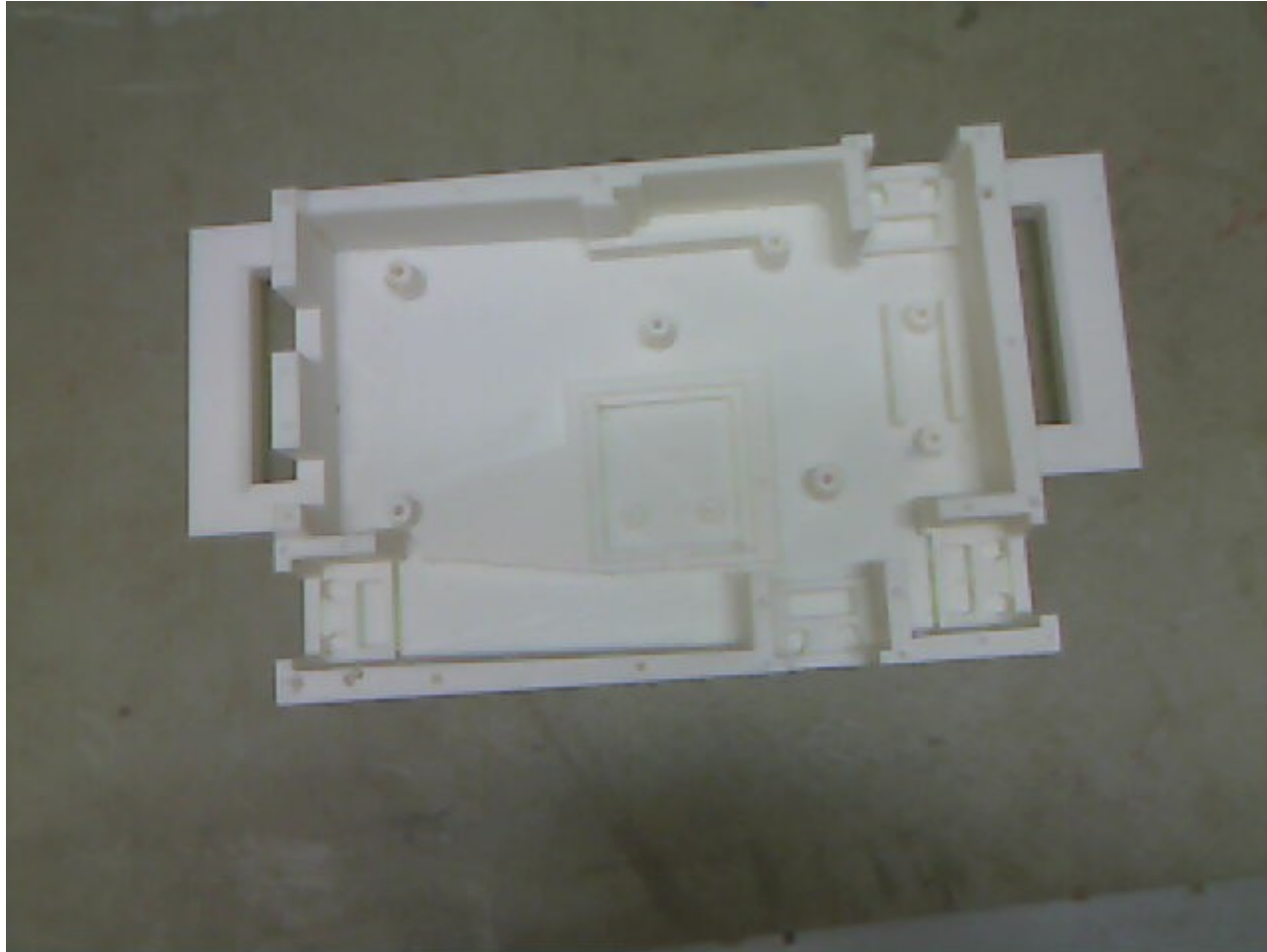


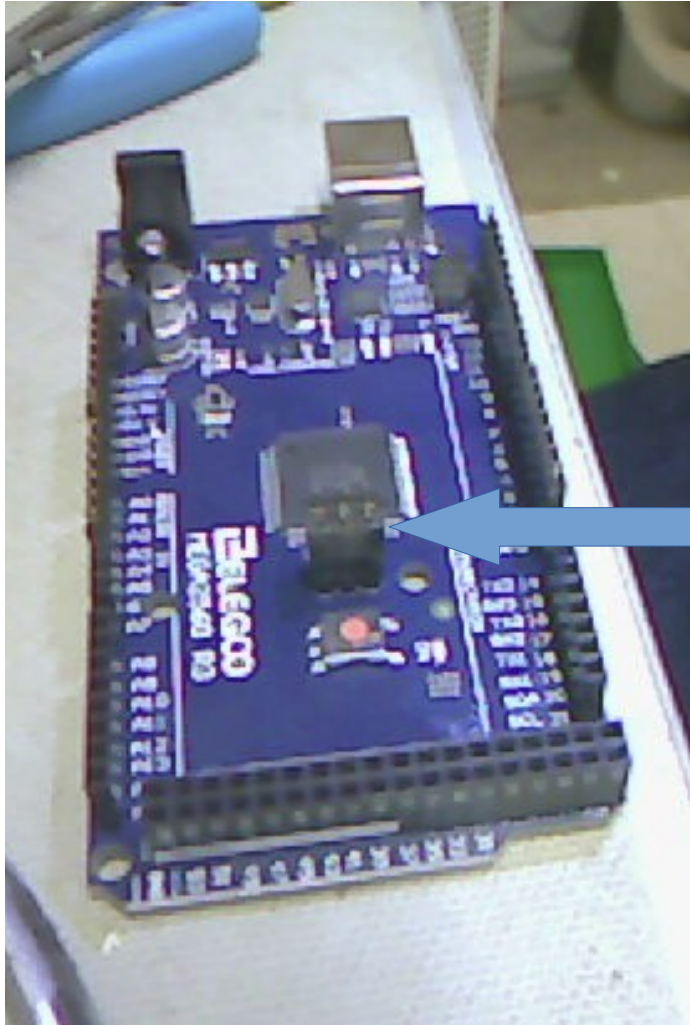Install all headers necessary to solder to the Adafruit Data Logging (sd card) shield into the Mega 2560 board.





Don't forget the female header on the center pins.

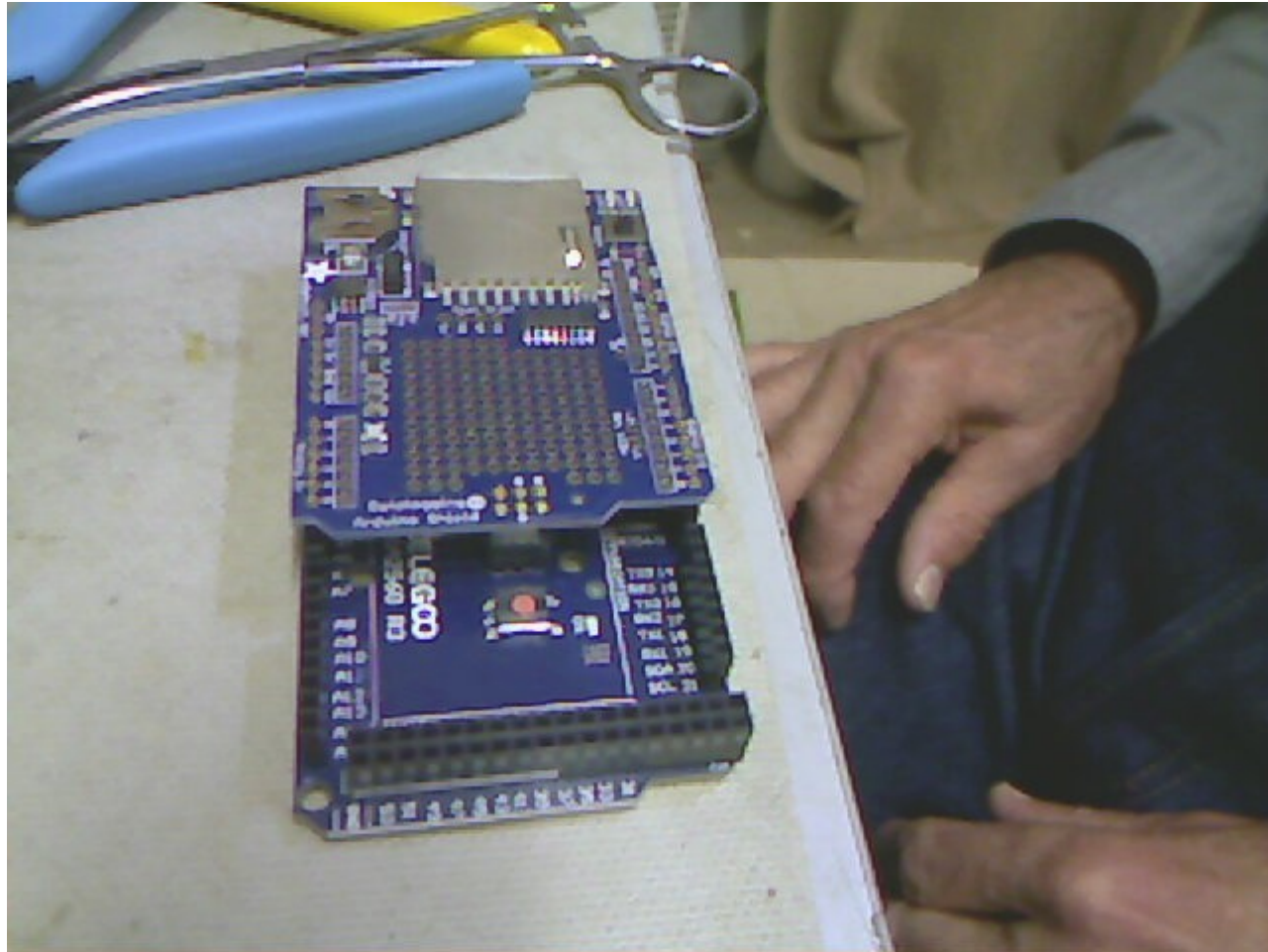Add the shield on to the 2560 and solder all of the headers in.





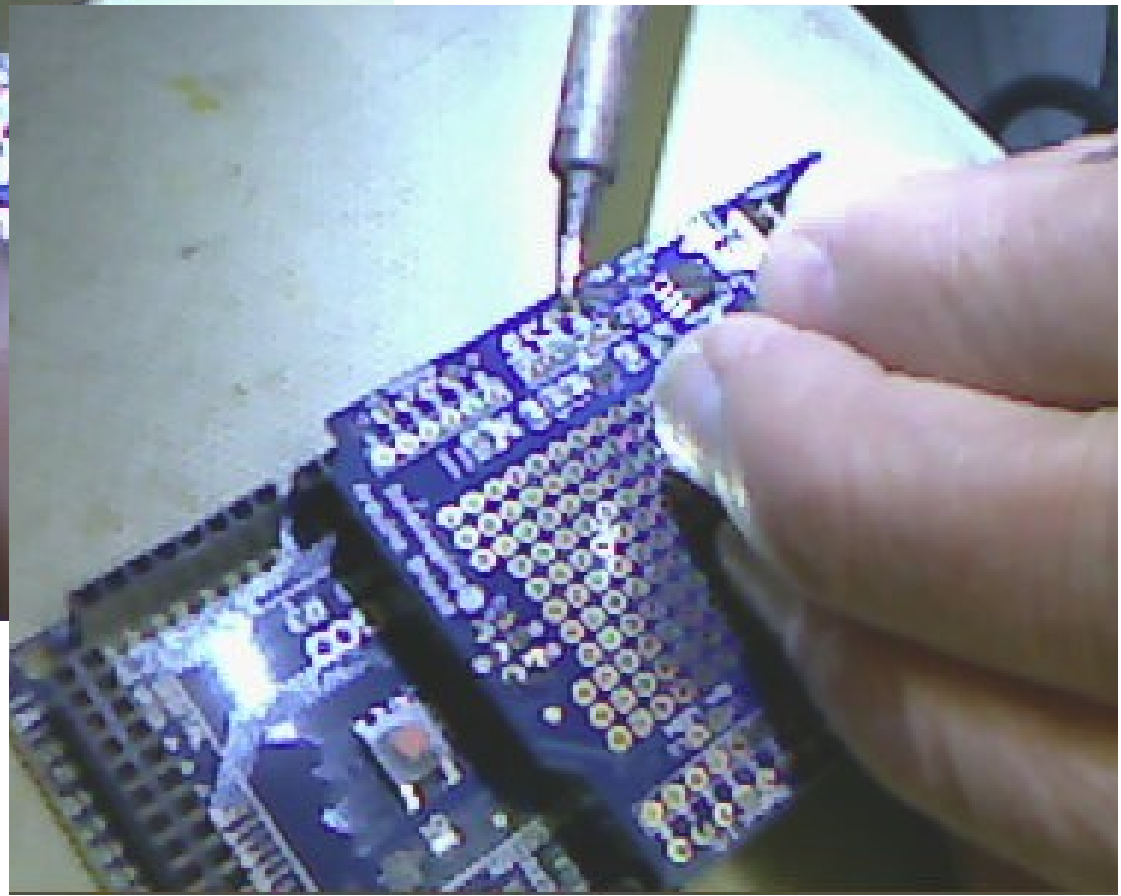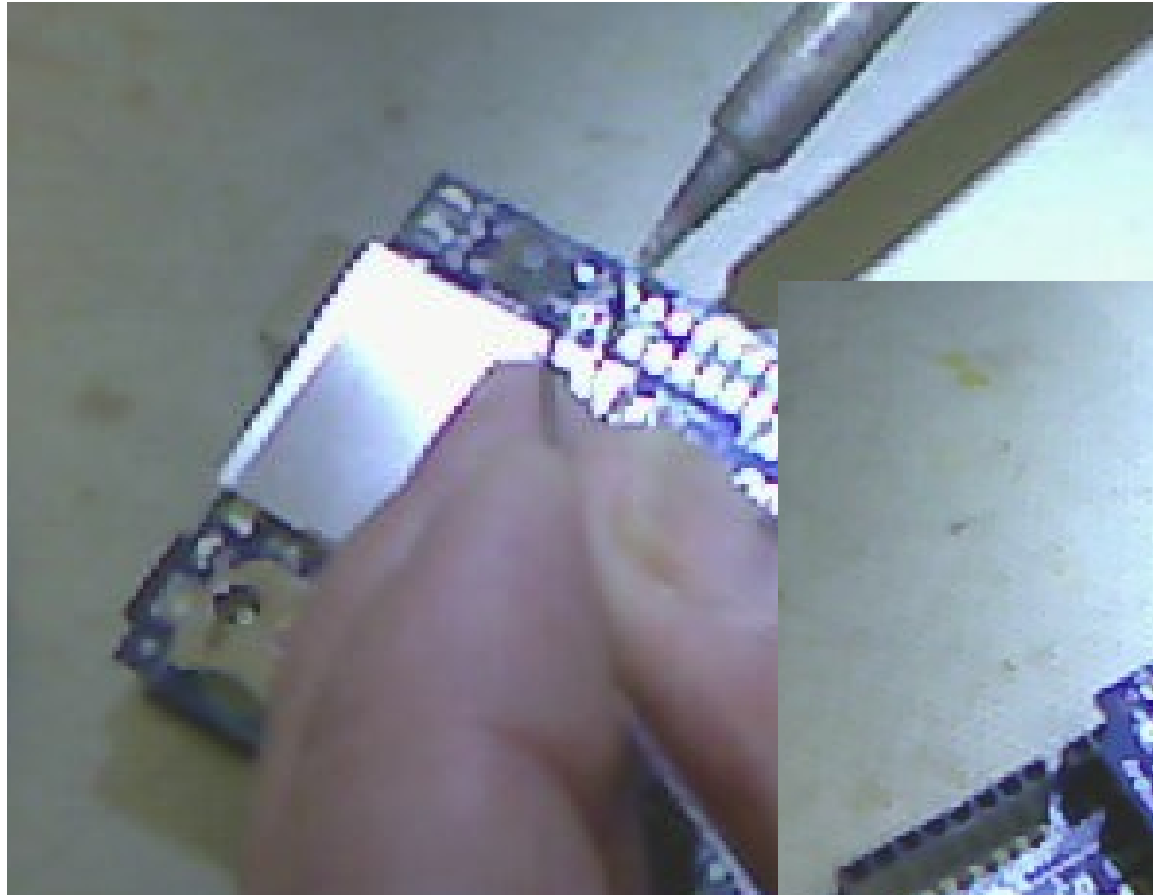Make sure and fully solder the pins on
all headers




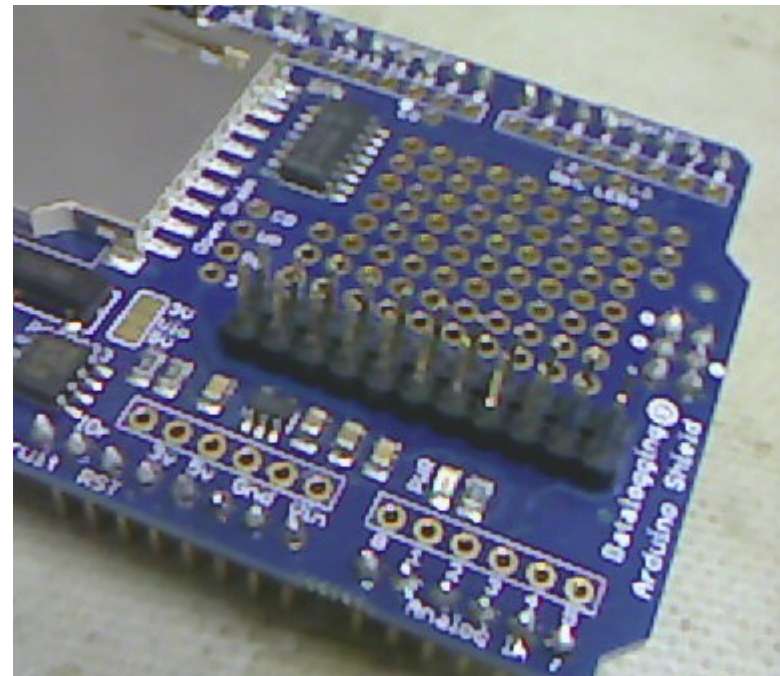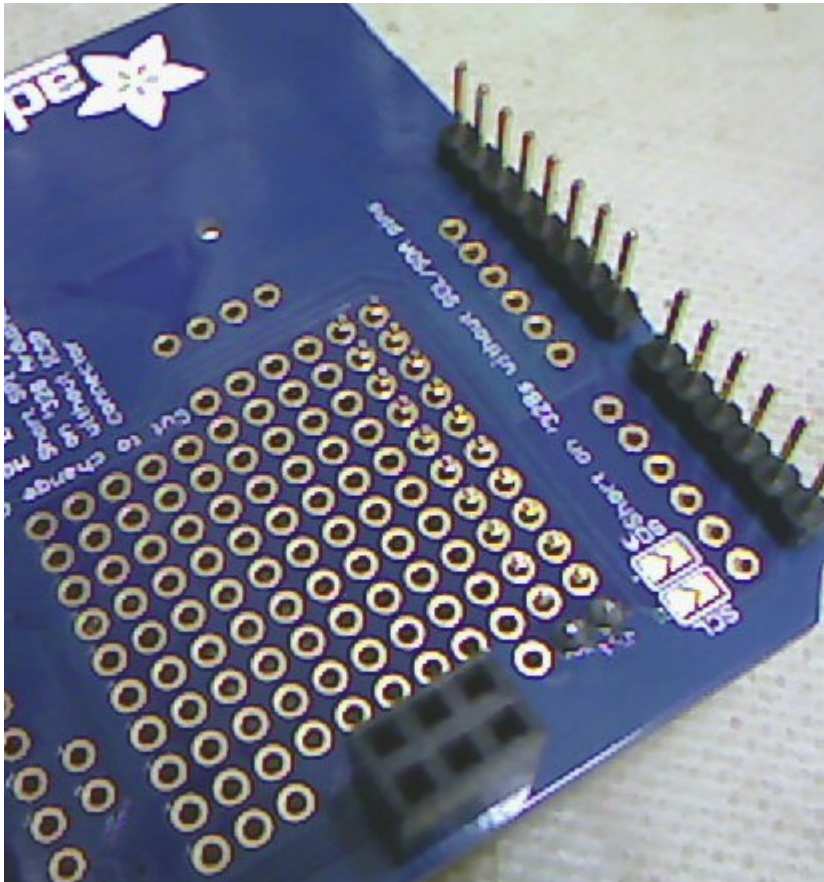3.3v and ground header (DO NOT USE 5V)


- Install two rows of headers as shown. Tack them in at each end with solder



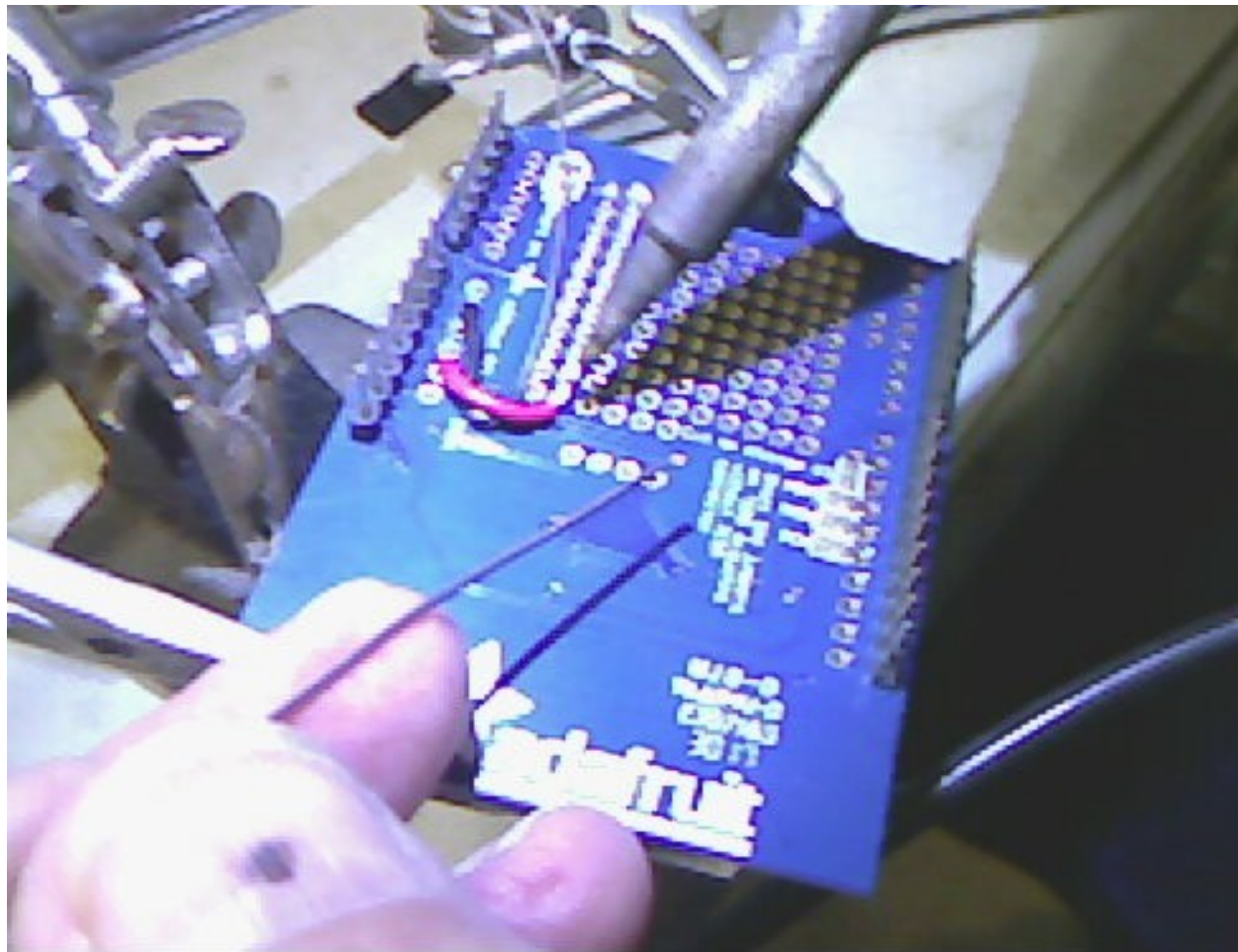
Solder a Red Wire up through the 3V hole and connect it to the row of header that is closest to the center of the board.



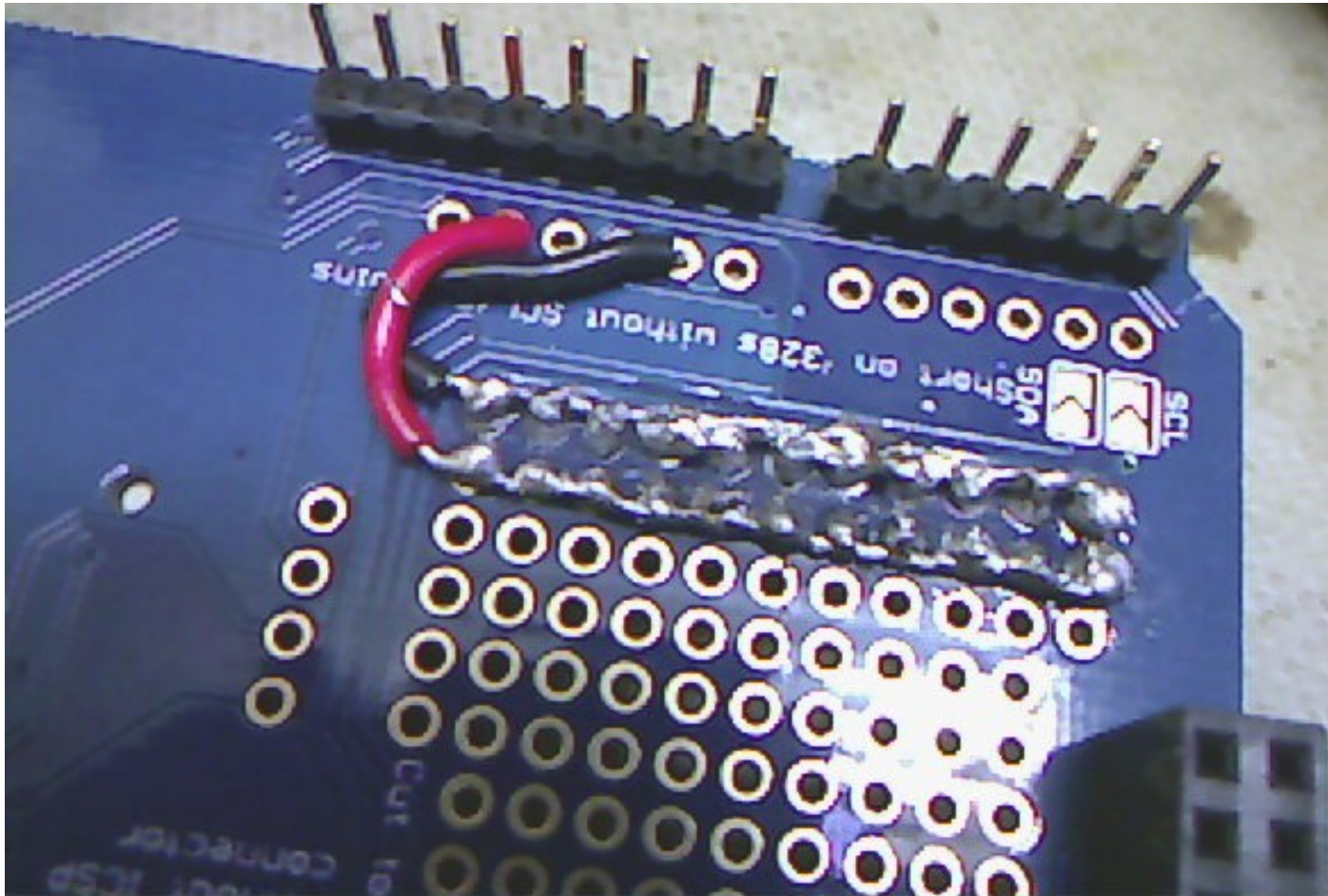
Connect a black wire through the Gnd hole and connect it to the row of pins closest to the edge



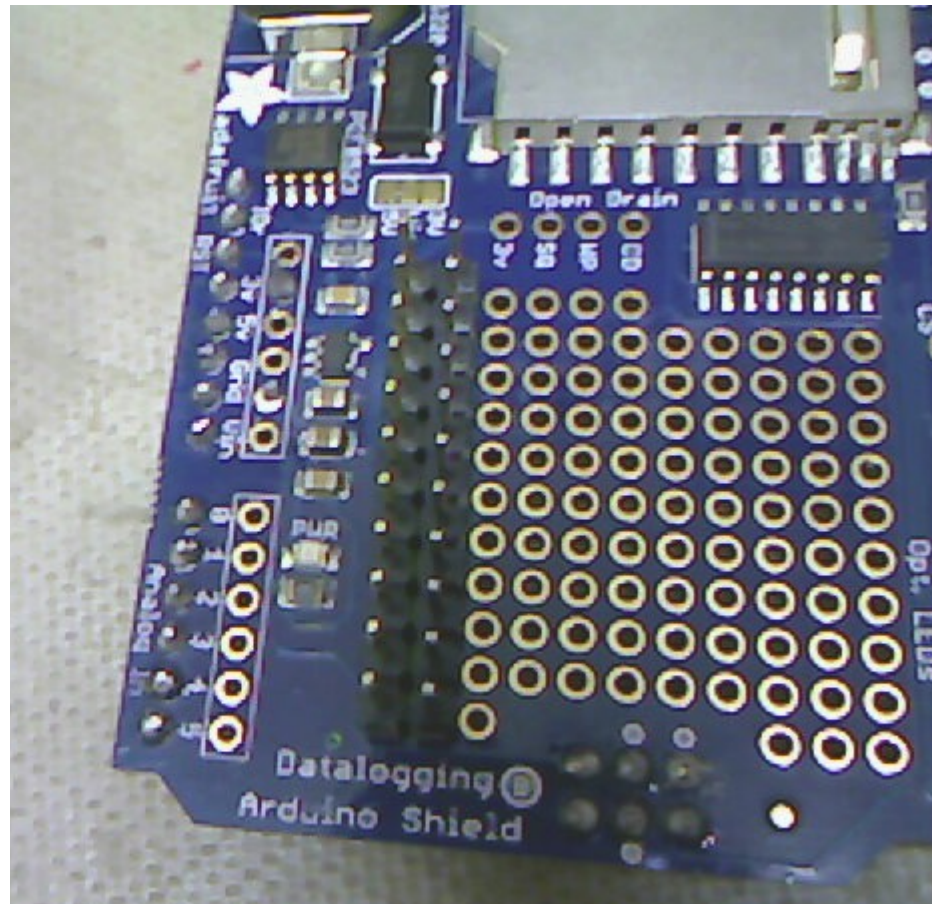
This is what the header looks like when done.




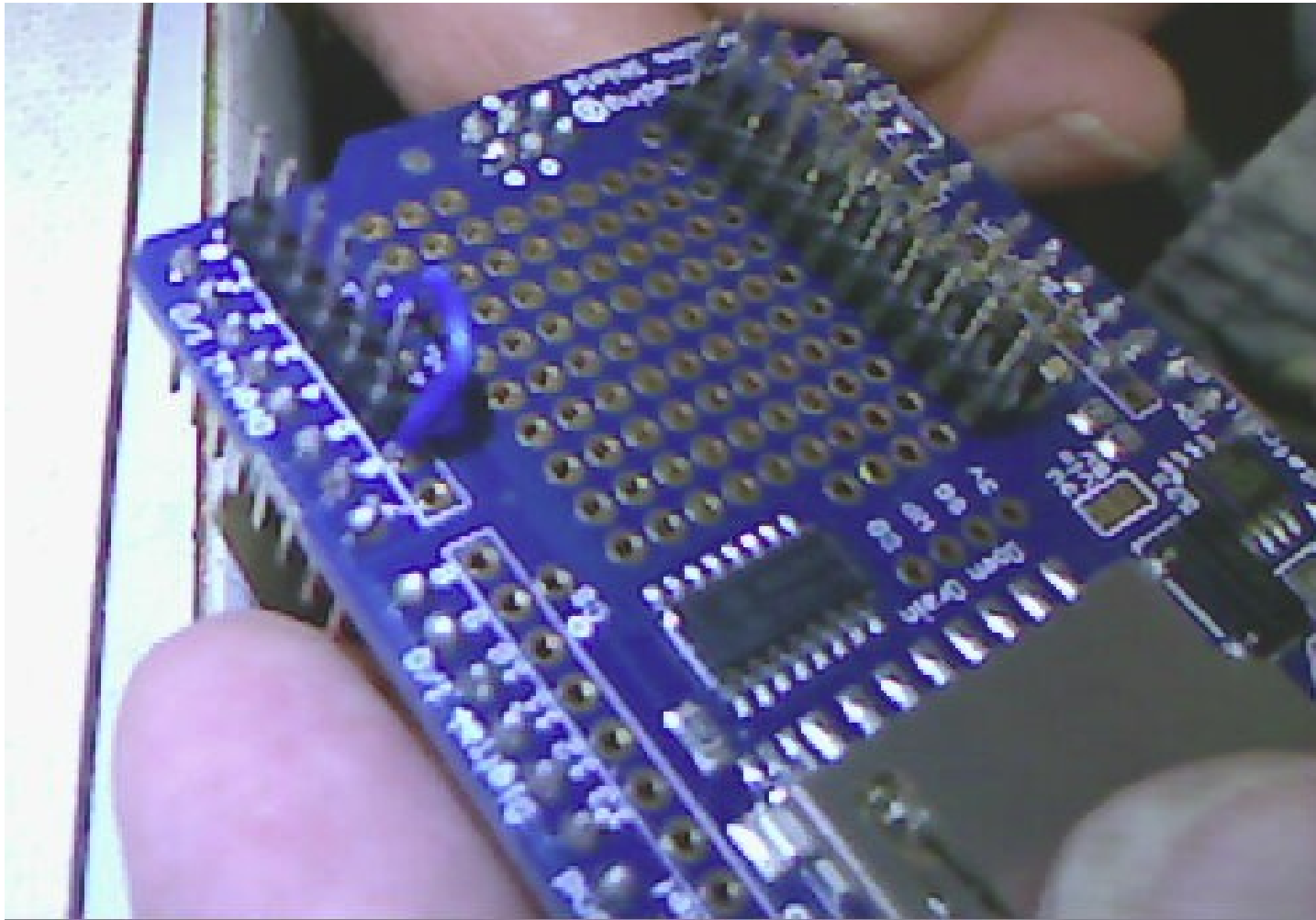
Solder a Header on pins 0-5 and
Solder a wire on the topside from L1 to
pin 6 on the Data Logging shield



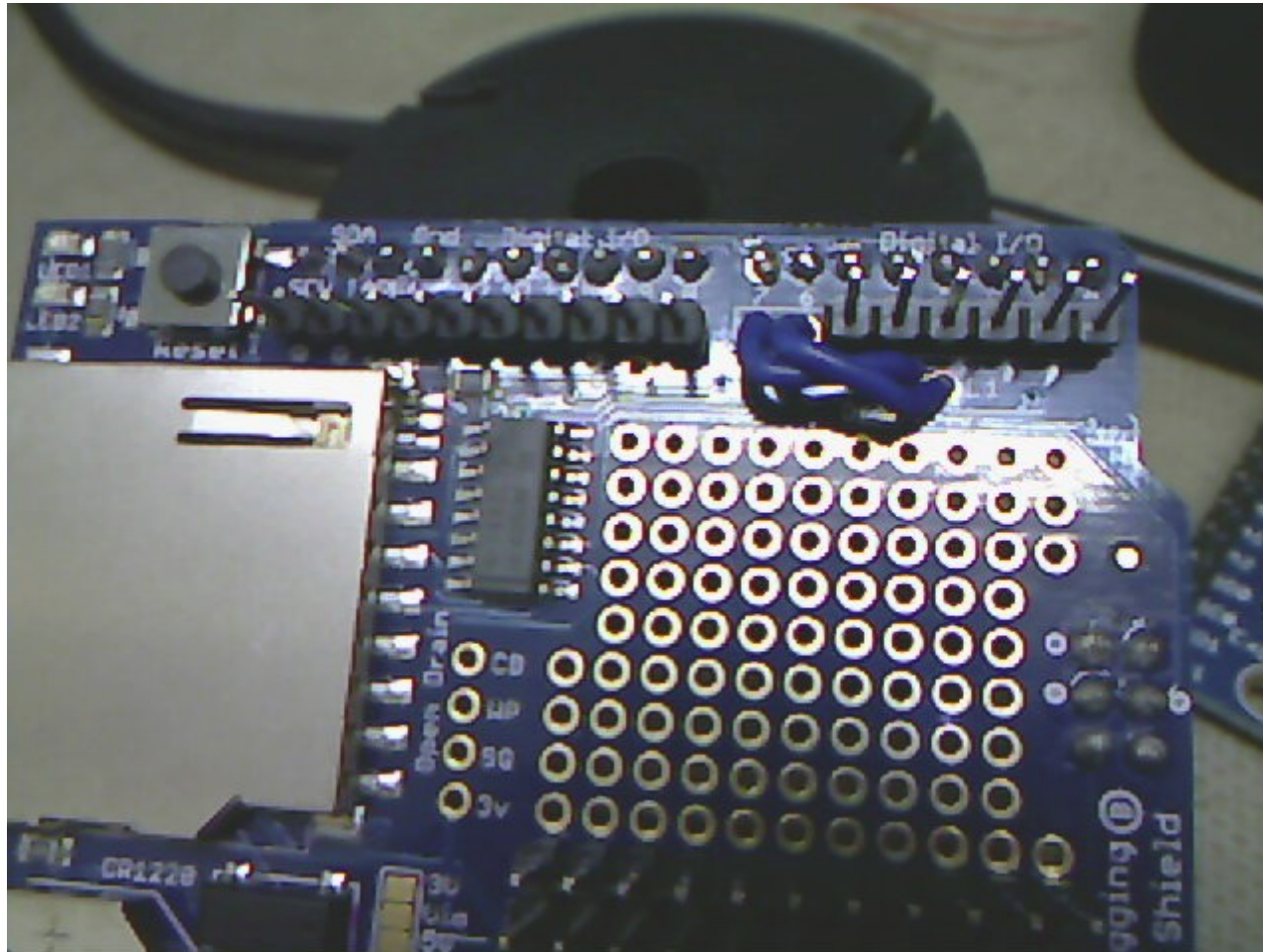
Put header on pins Sclk through 8 and
Solder a wire on the topside from L2 to
pin 7 on the Data Logging shield



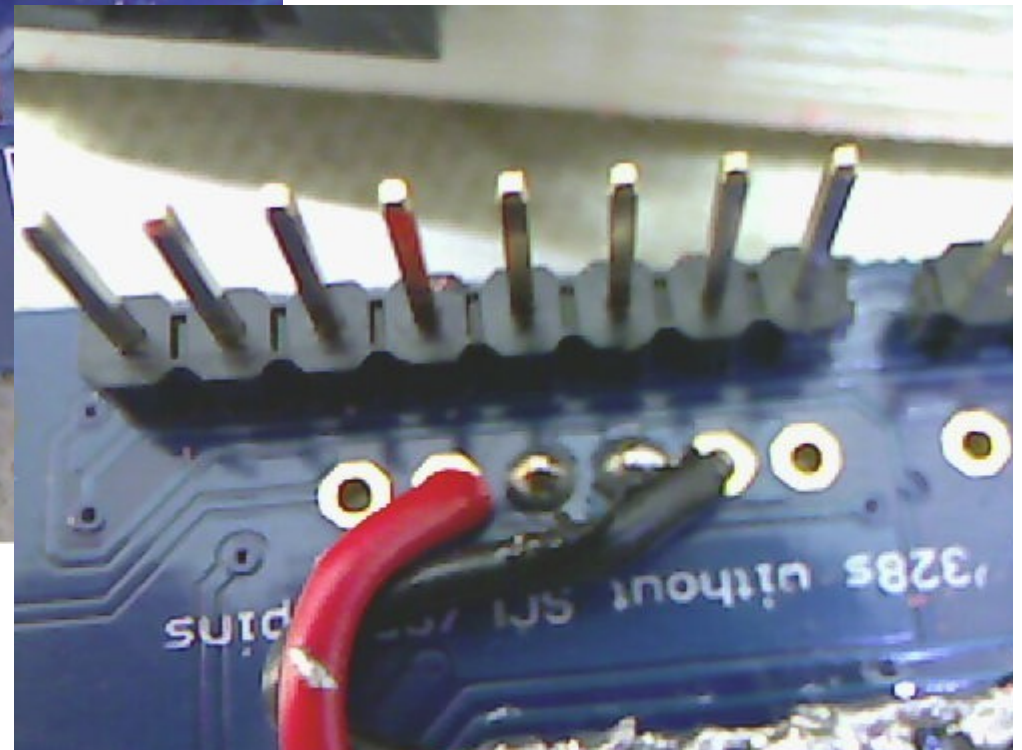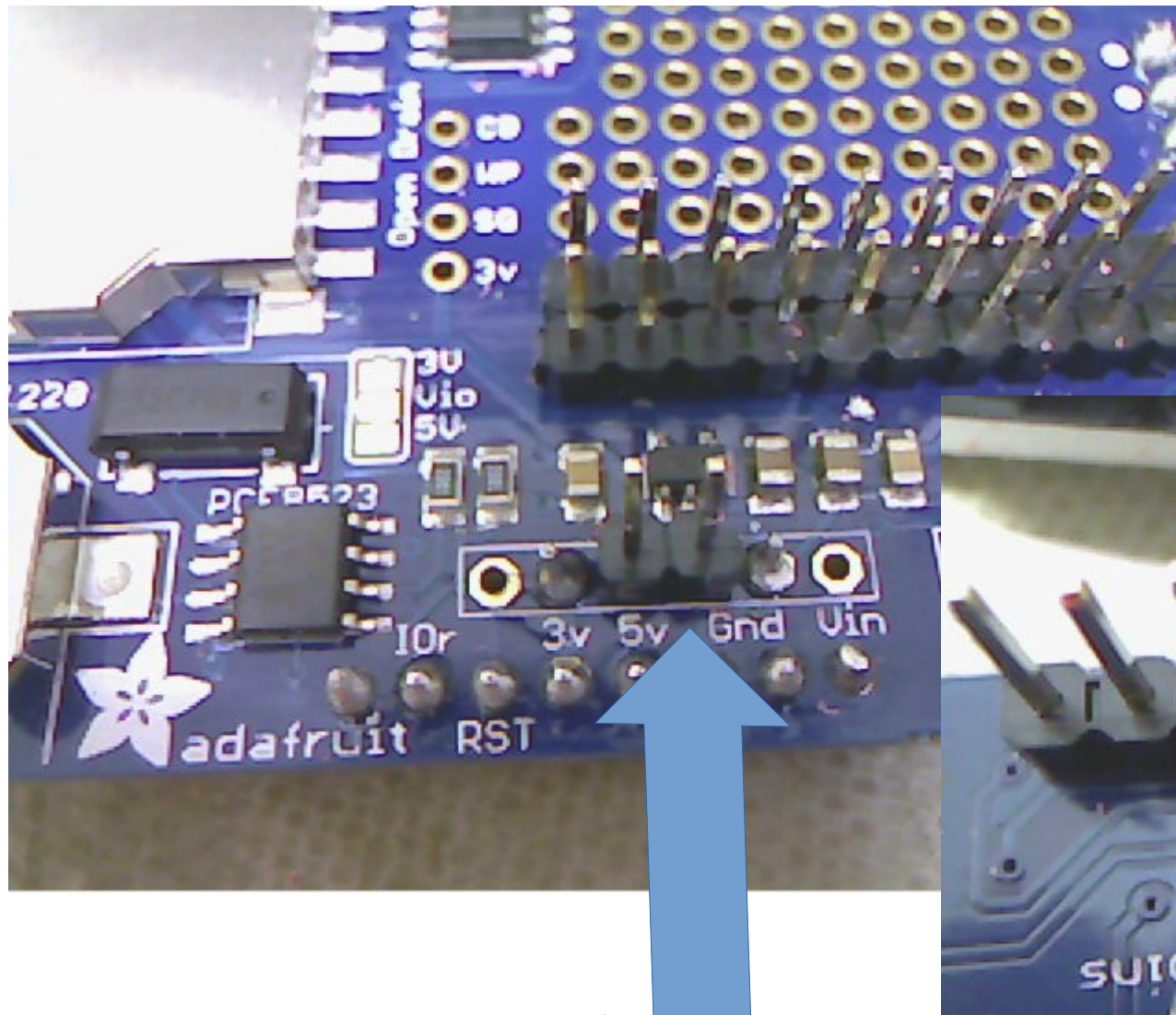- Install a 2 pin header on 5V and Ground as shown. Solder from the back side.



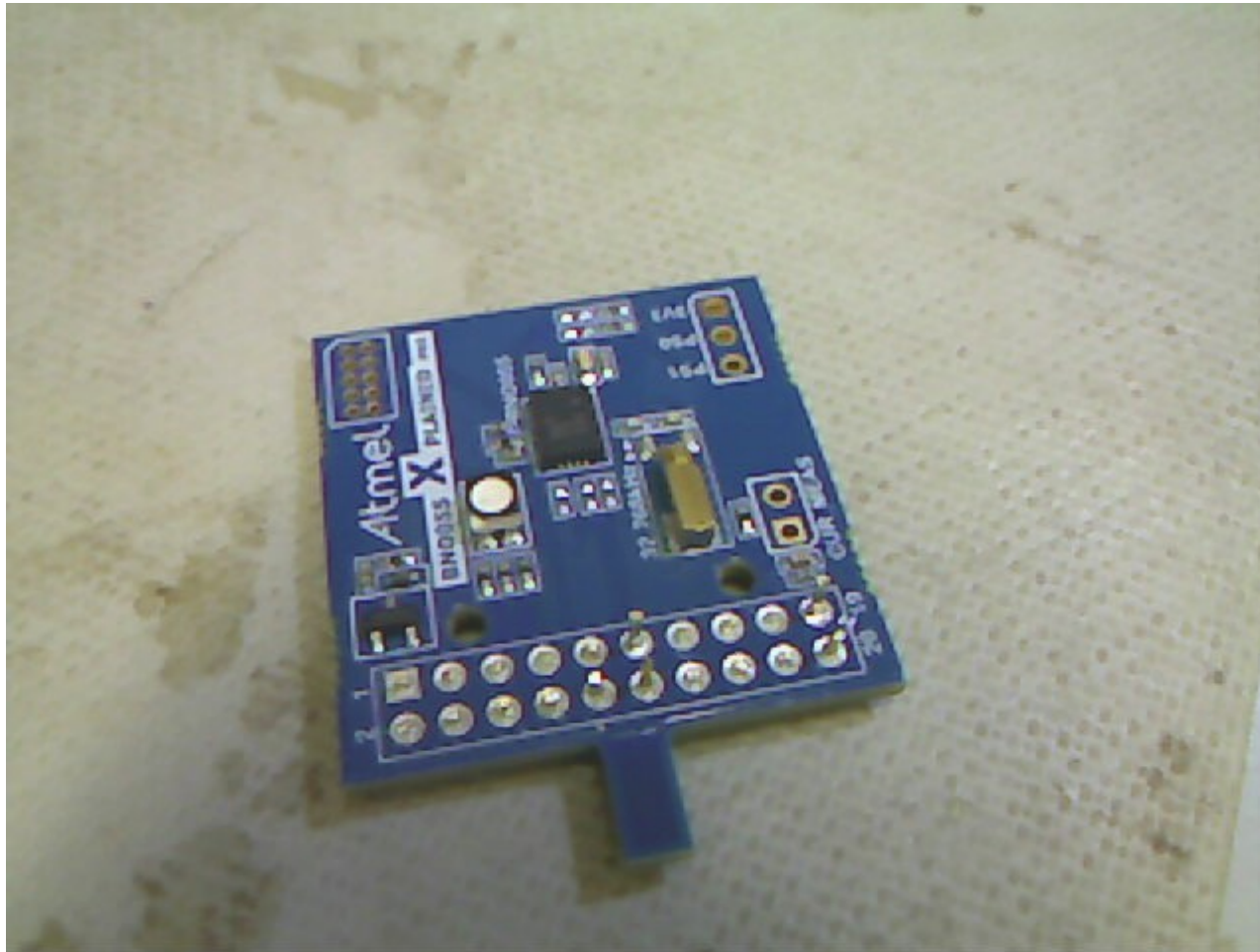
Clip all pins on the IMU flush except
11,12,19 and 20.




Solder four stranded wires 4-5 inches
long:
red-20,black-19,white-12,yellow 11.





Install Arduino Mega 2560

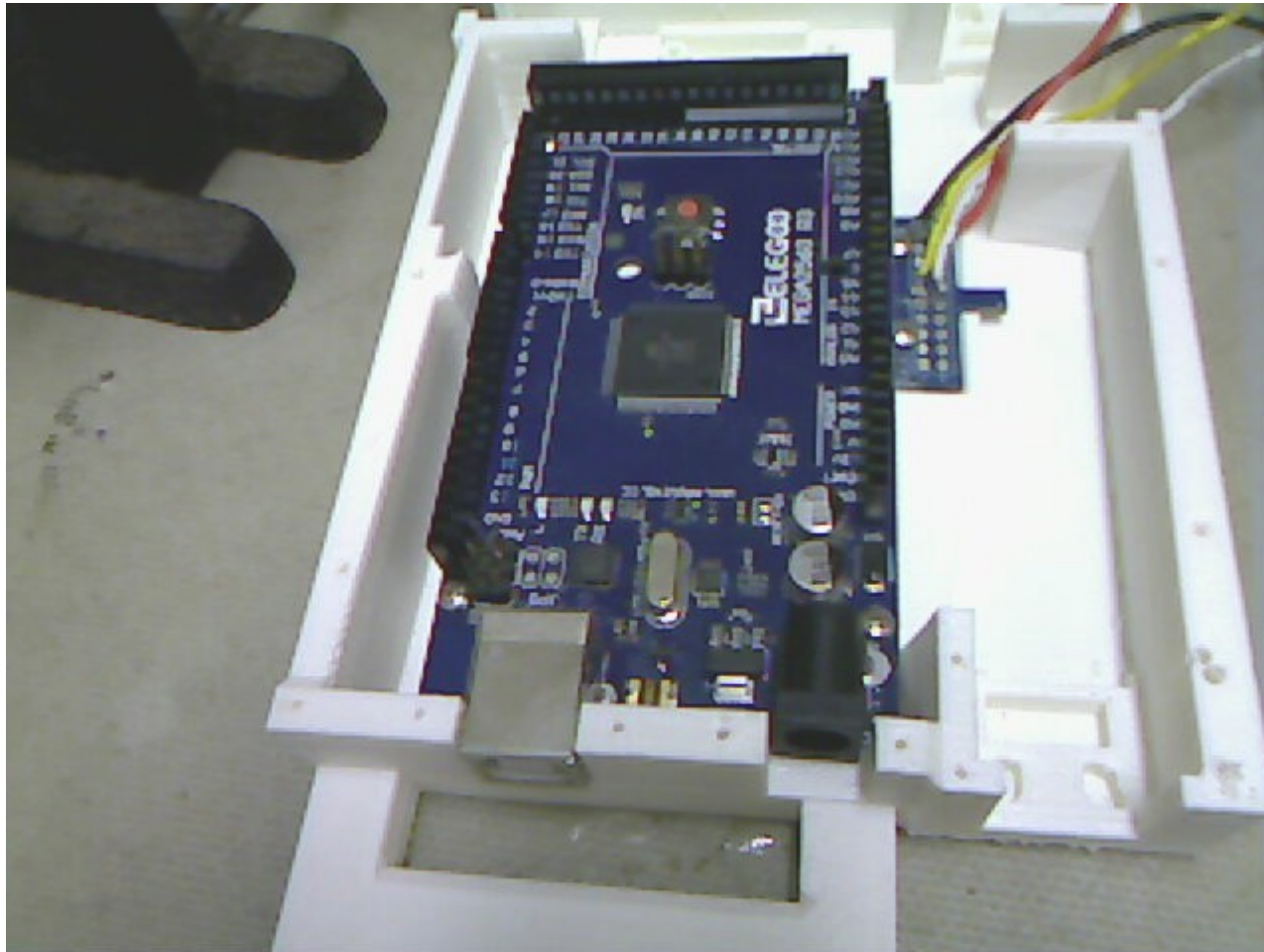

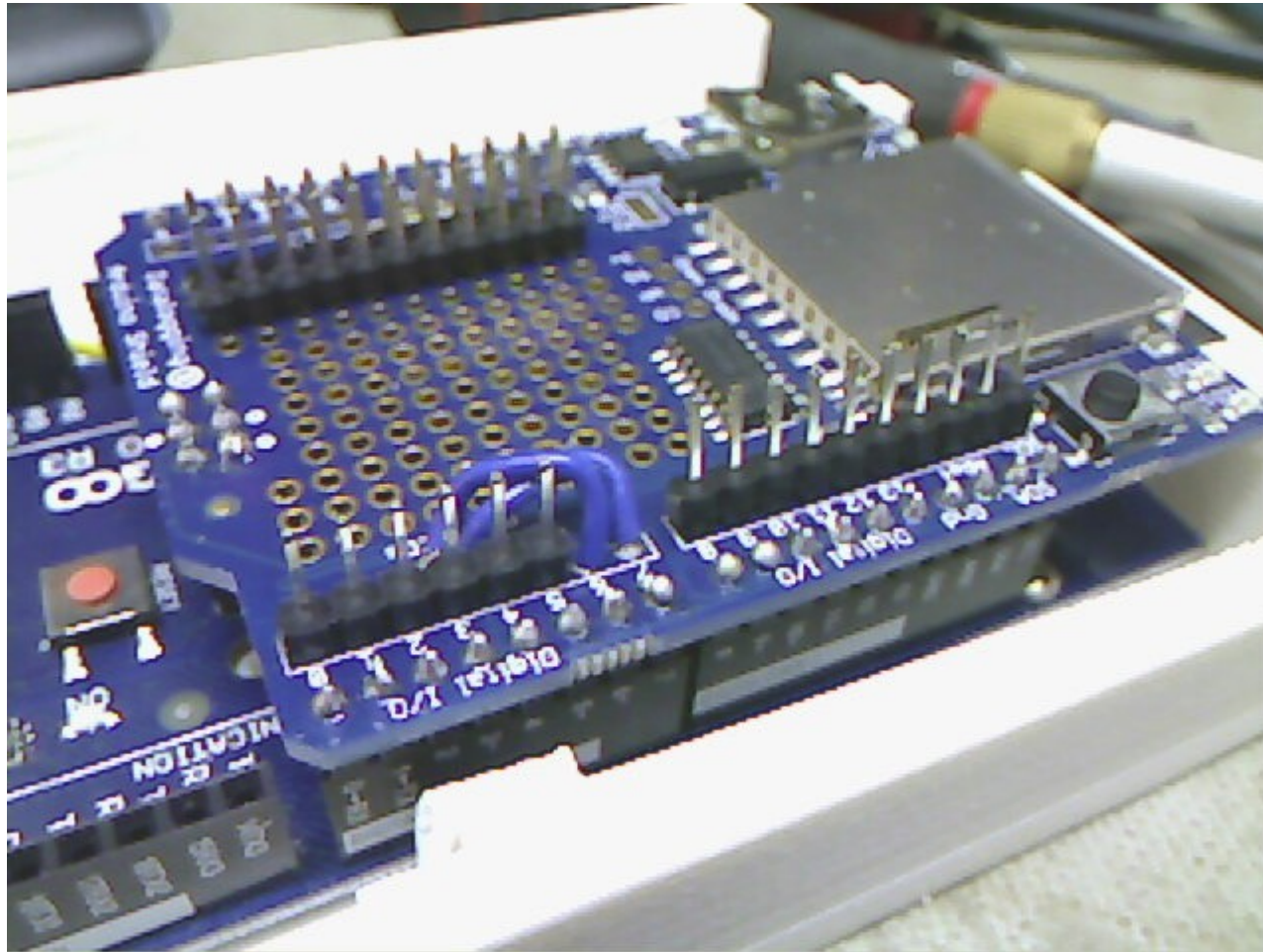
Install Data Logging Shield on to Mega 2560 (line up male females as shown)



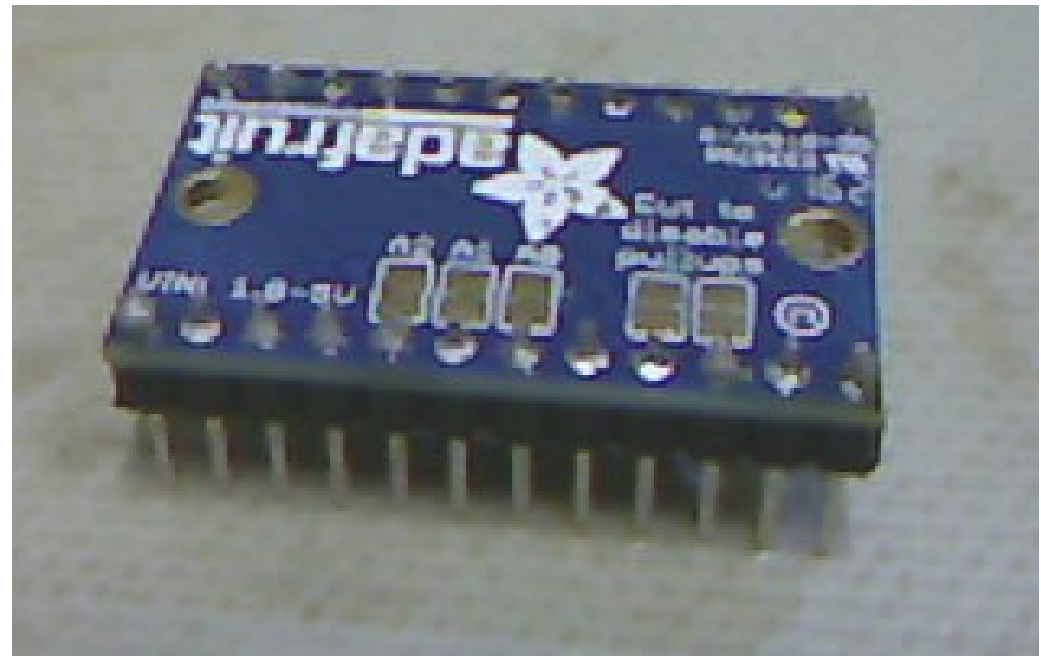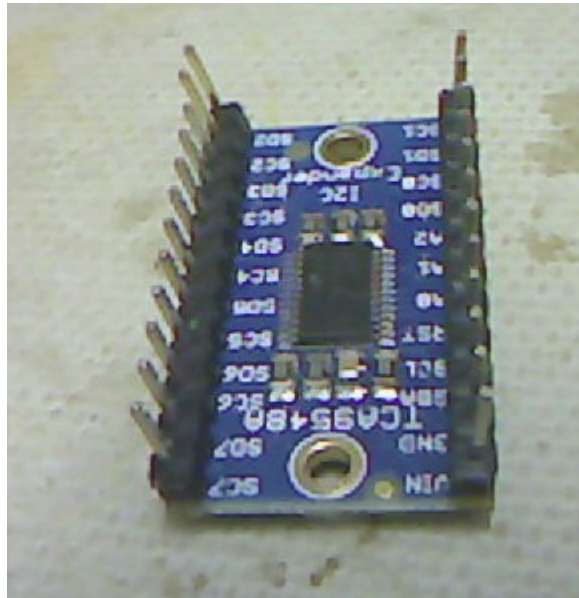Solder in vertical headers on i2c multiplexer.



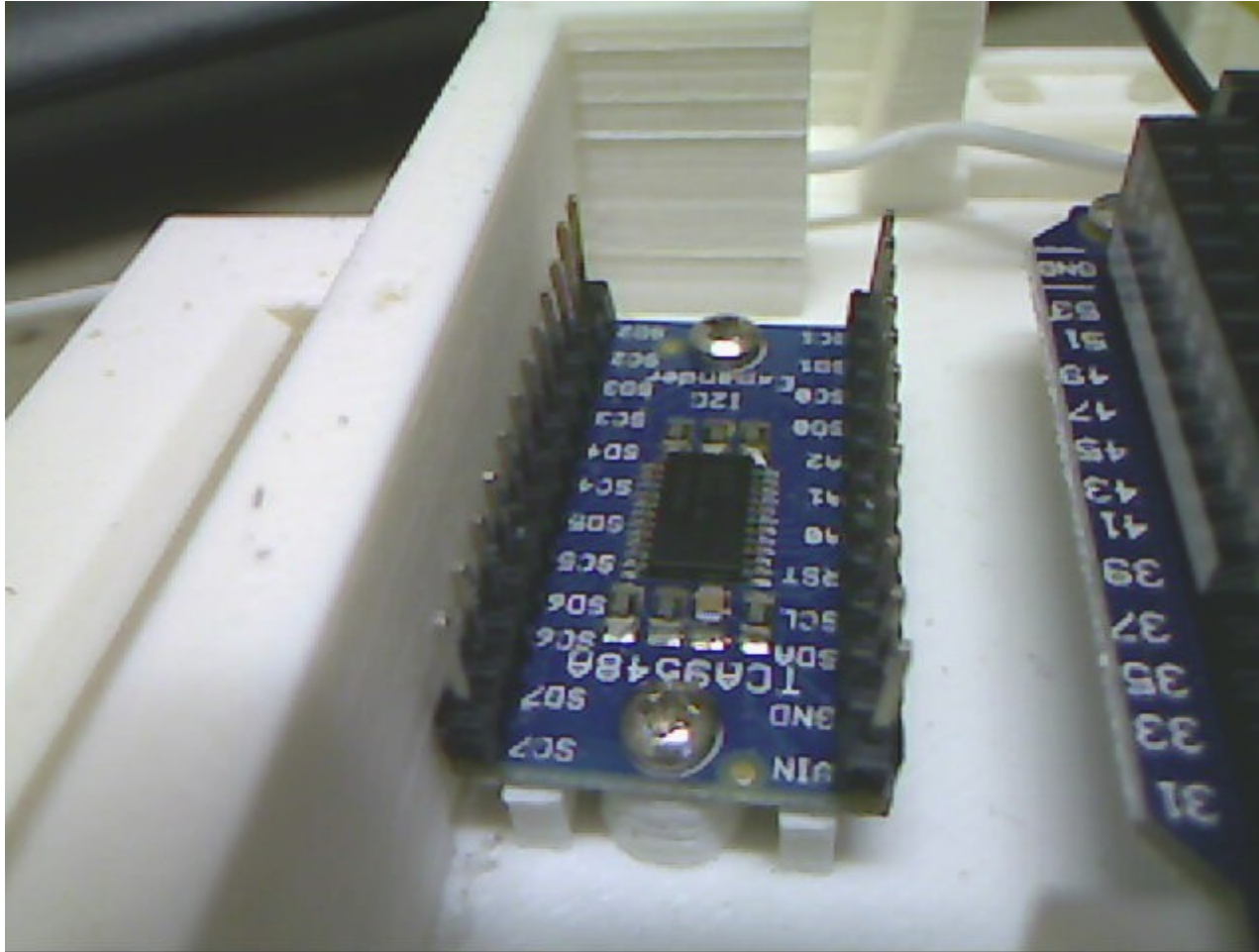Install I2C Multiplexer into assembly as shown (note orientation).




Make four Ethernets with headers on them as shown




Epoxy the four Ethernet into their locations in the assembly

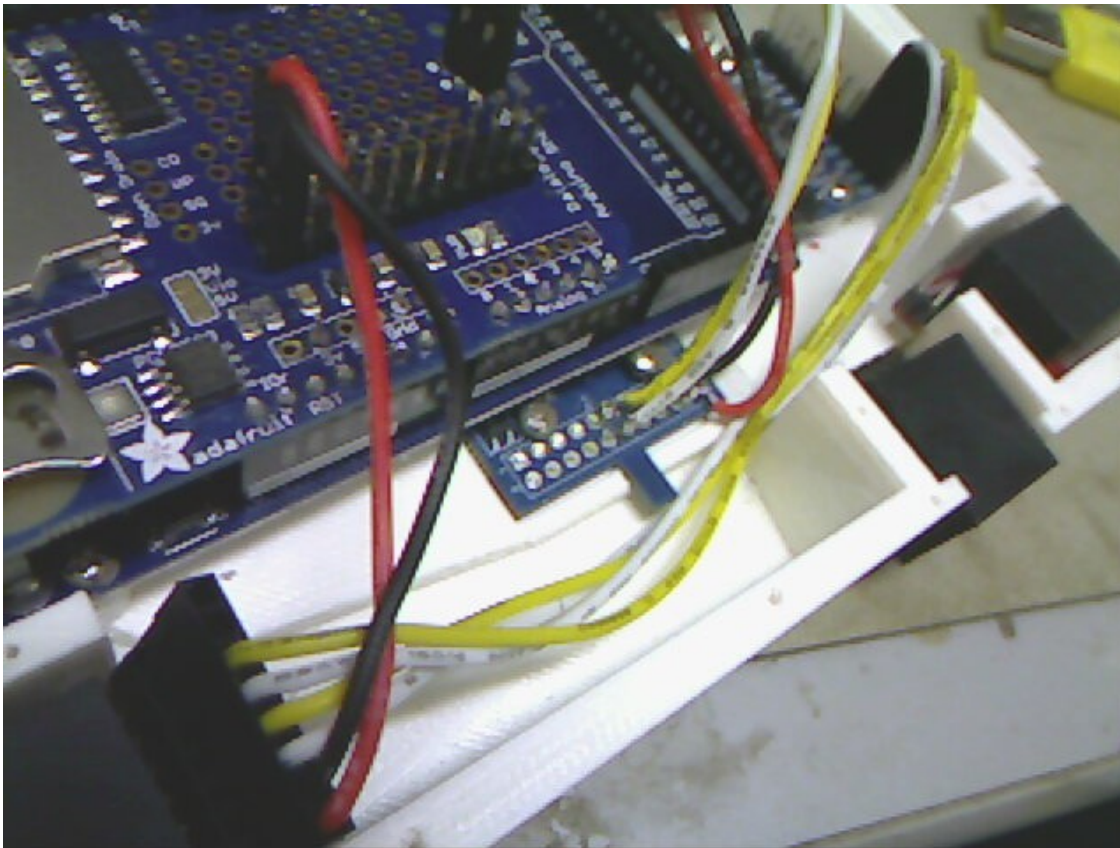- Start a Harness On the Upper Left Arm Connector. Create two wires for power and four wires for SDA and SCLK.




Finish the Upper Left Harness by connecting it to SD2, SC2, SD3, and SC3 as shown

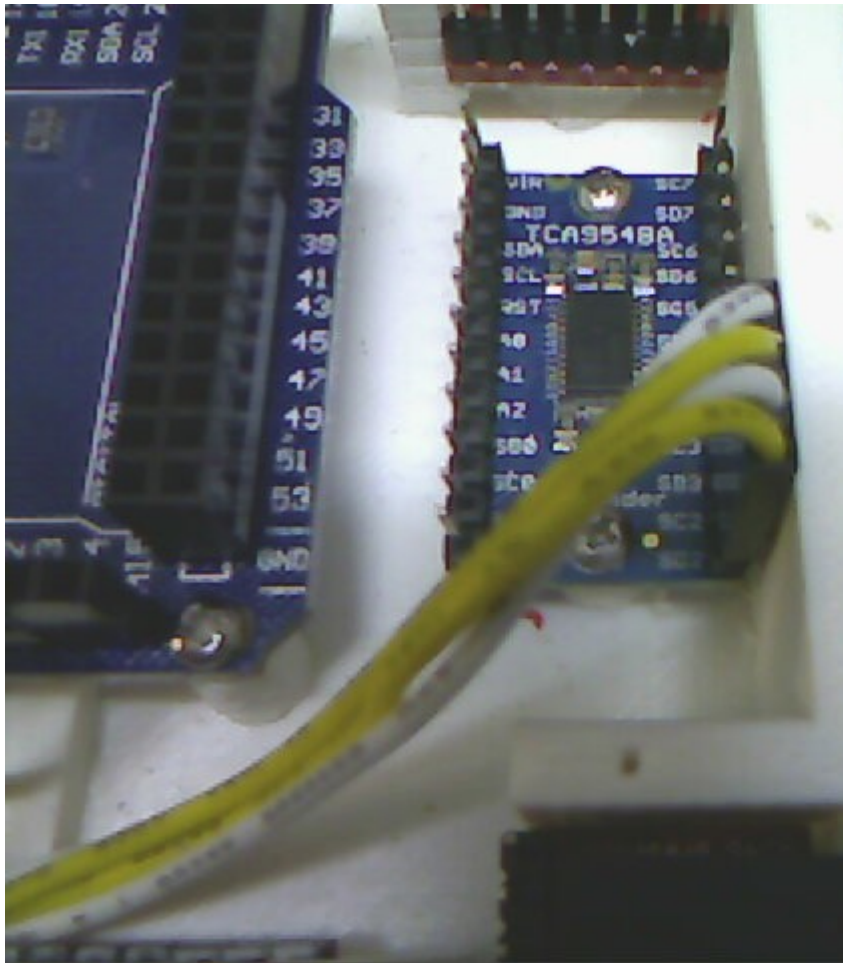- Pin 3 white of the Ethernet goes to SC2,
- Pin 4 yellow goes to SD2,
- Pin 5 white goes to SC3 and
- pin 6 yellow goes to SD3.




Put two two pin terminals on the wires coming off of the IMU that we put in previously.

Red always goes on the center rail.

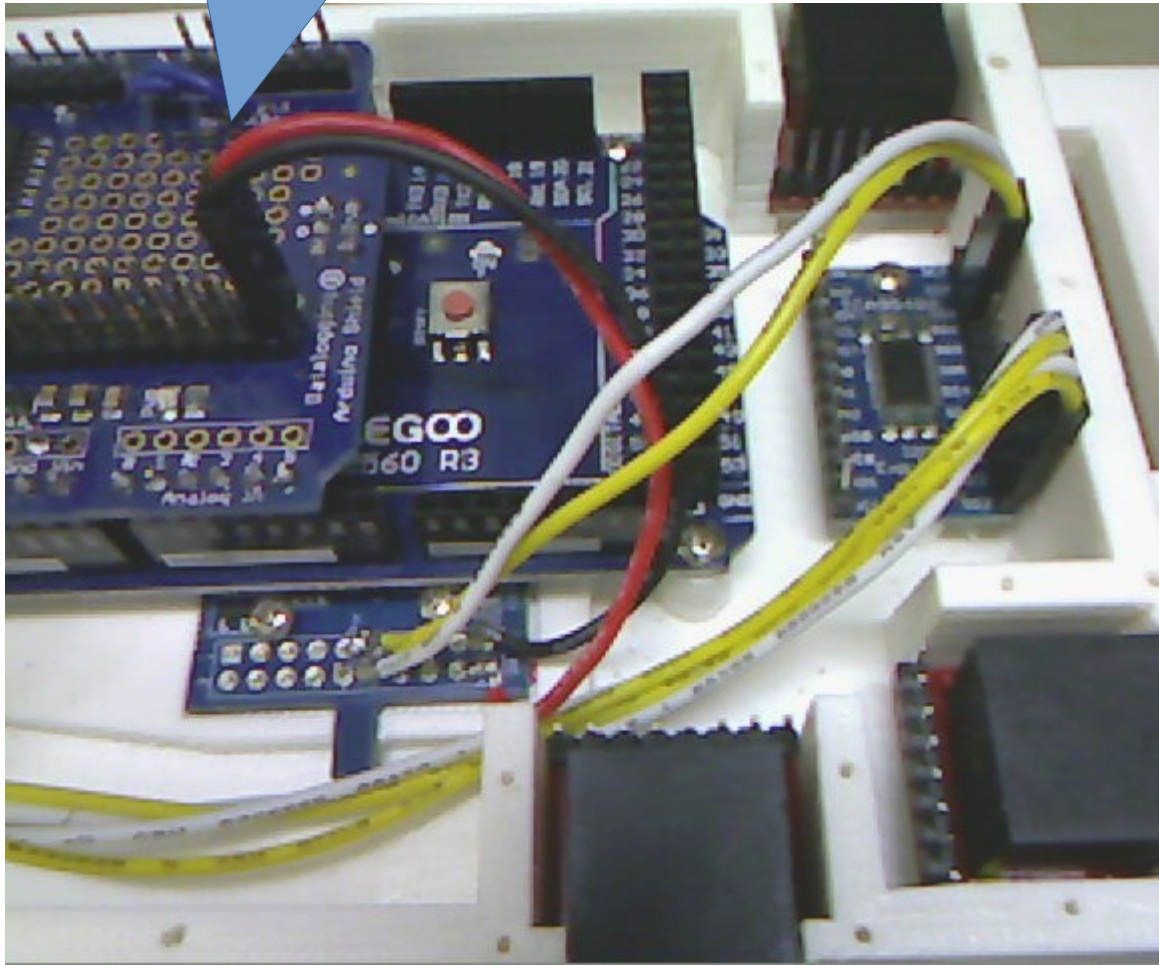


- Connect the wires as shown. Red and black go to Power and Gnd as shown.
- 12 white goes to SD6 and
- 11 Yellow goes to SC6.

Create the head harness

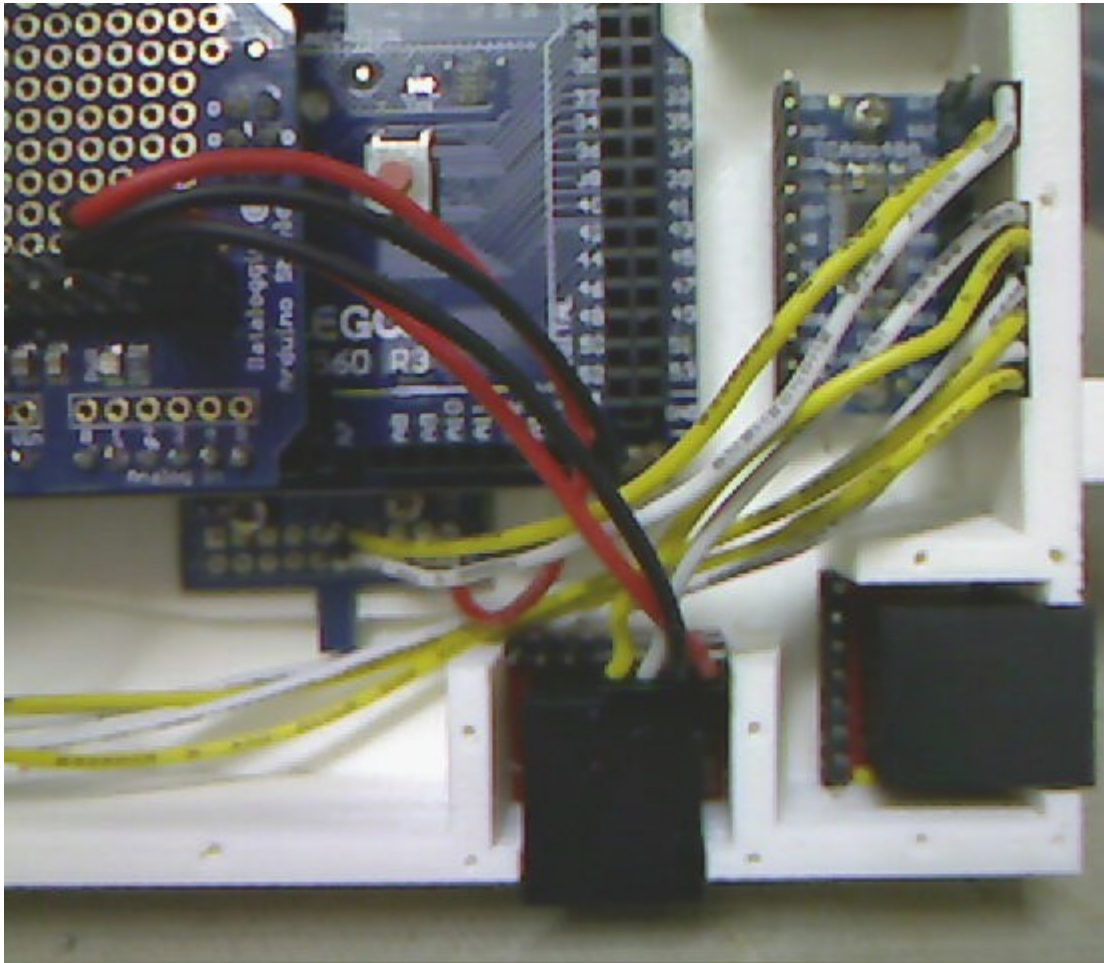


- Create a four pin header that connects to the head ethernet as shown. Pins 1(power) and 2(gnd) go to the power header on the data logging shield. Pin 3 white goes to SC4 and Pin 4 yellow goes to SD4. (as shown


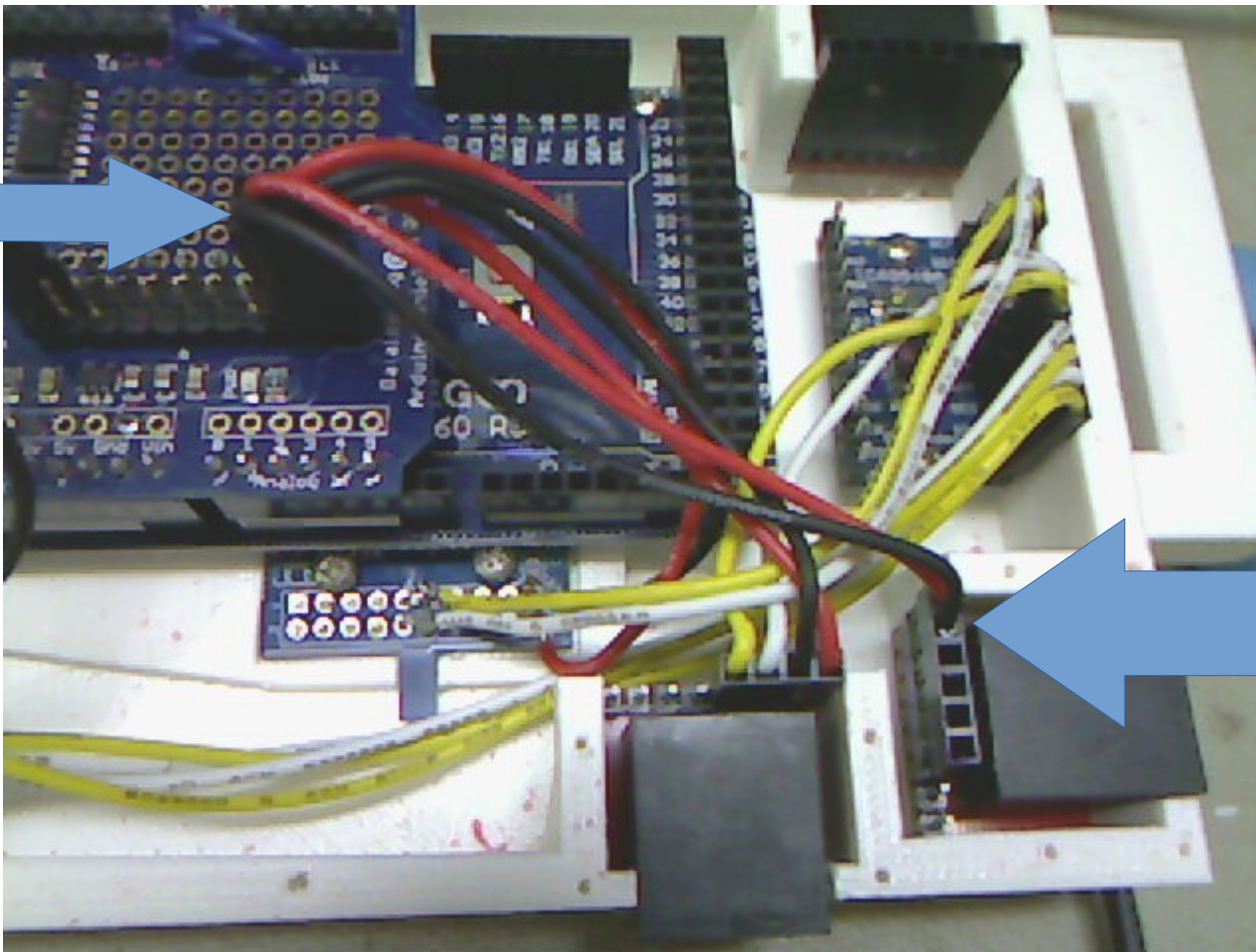
- Wire up the Right Arm. Put a Red on Pin 1 and Black on Pin 2. Place a two pin header on them and connect them to the power rail header on the data logging shield.



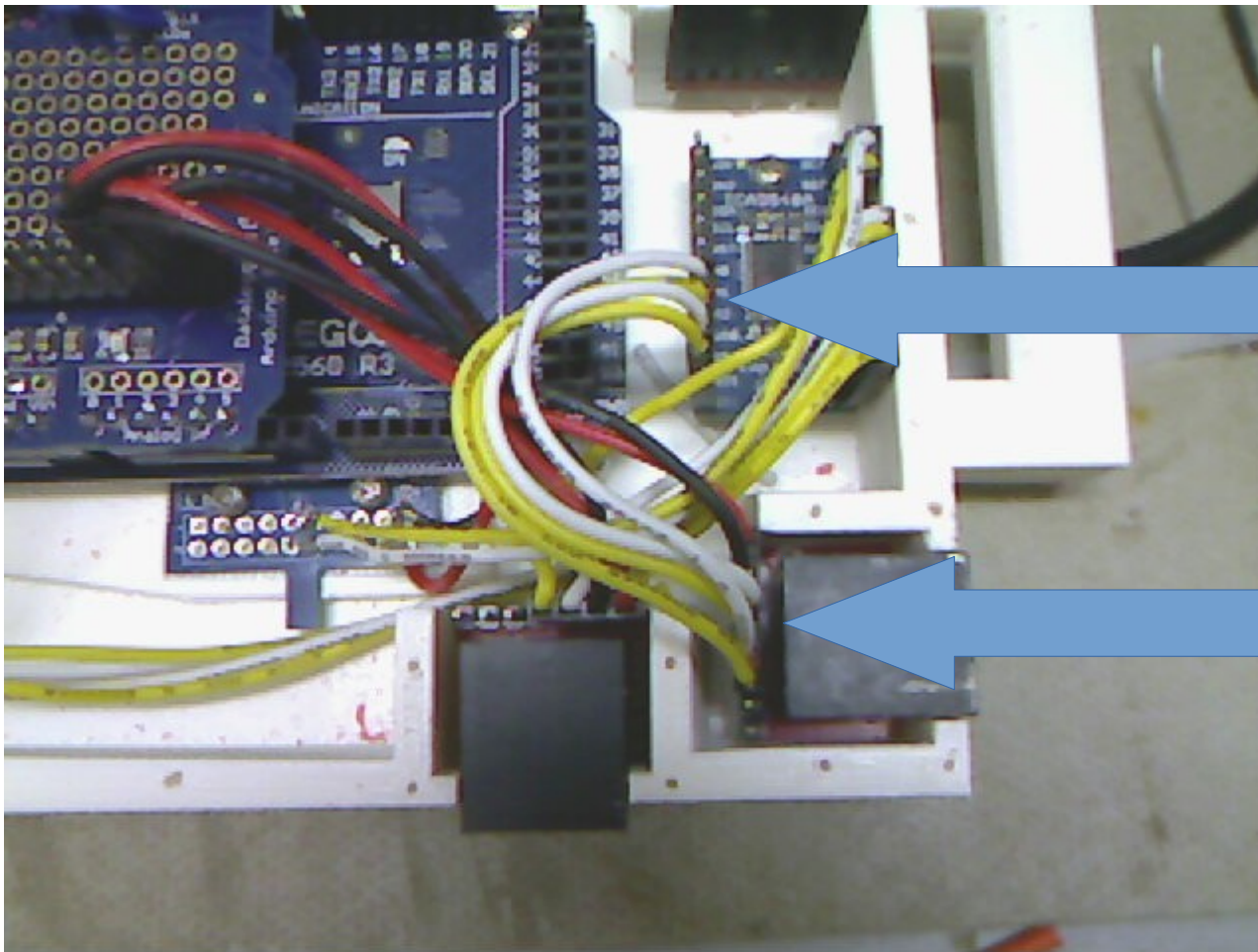
- Pin 3 White goes to SC0.
- Pin 4 Yellow goes to SD0
- Pin 5 White goes to SC1
- Pin 6 Yellow goes to SD1



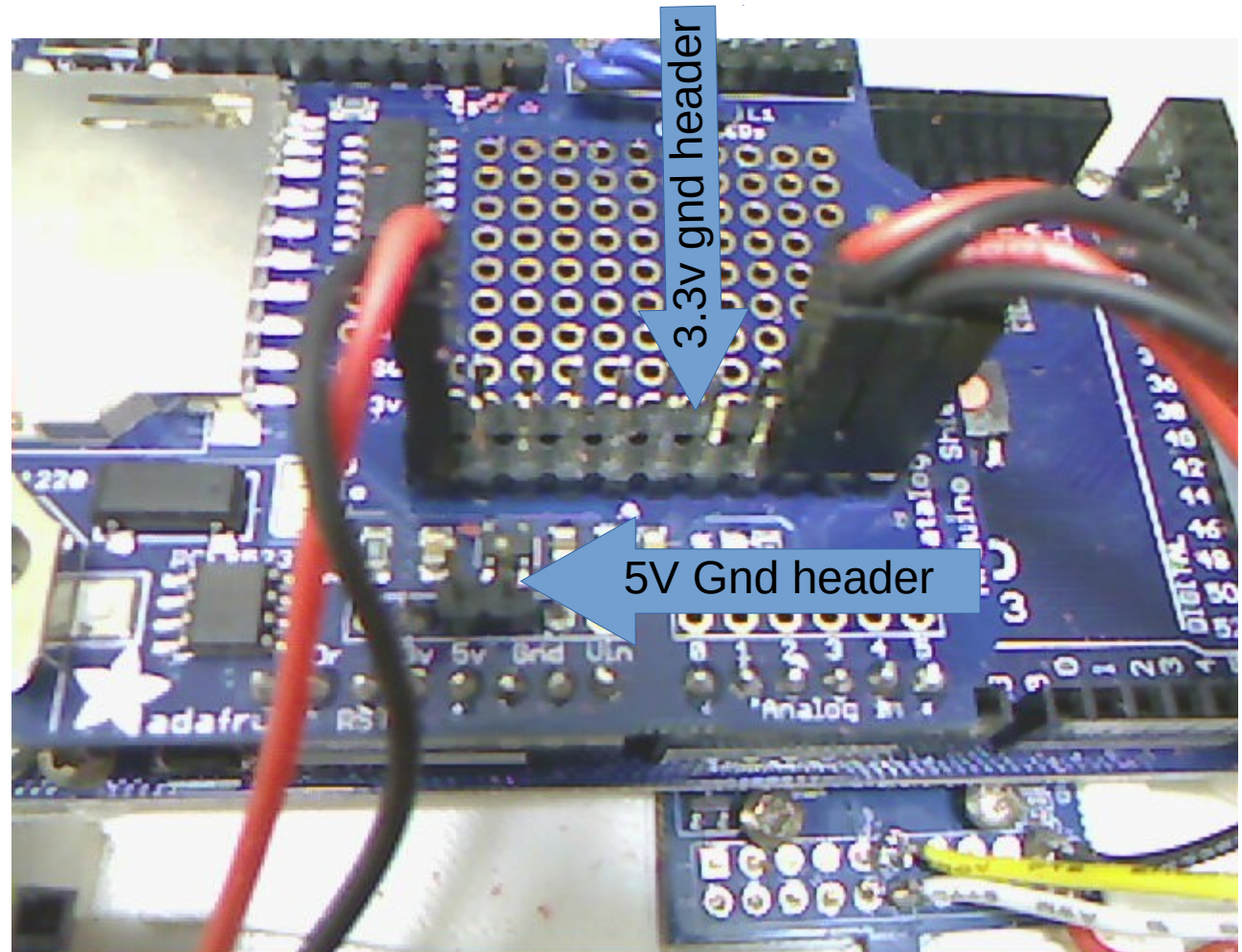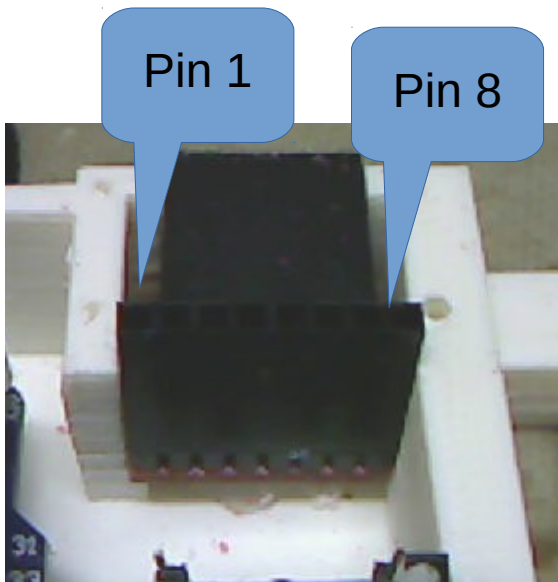
- Create a harness for the waist.
- Pin1 Red goes to 3.3v header.
- Pin2 Black goes to 3.3v ground header
- Pin 7 Red goes to 5v on two pin 5V Gnd header
- Pin 8 Black goes to Gnd on two pin 5V Gnd Header




- Wire the waist power as shown.

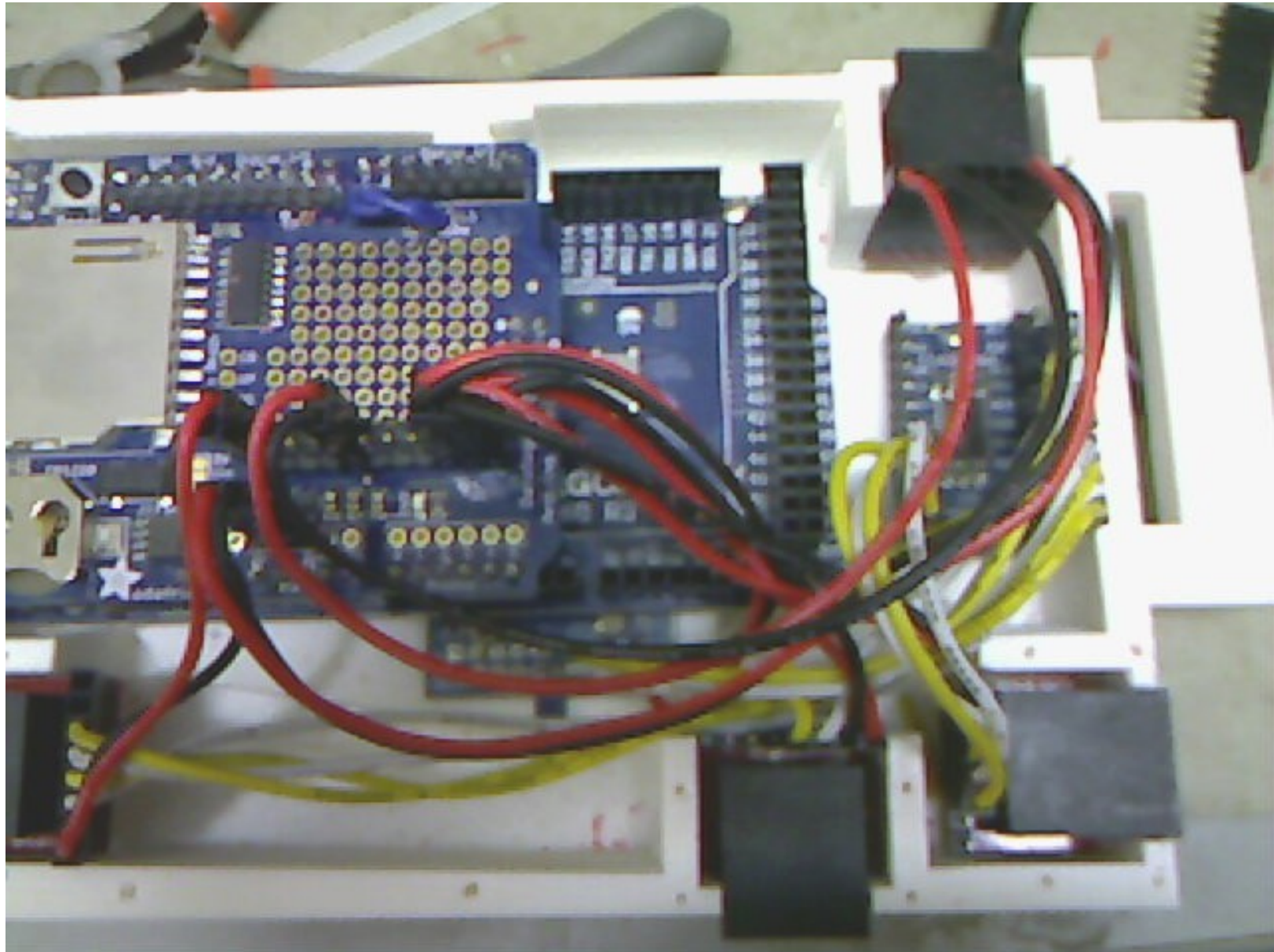

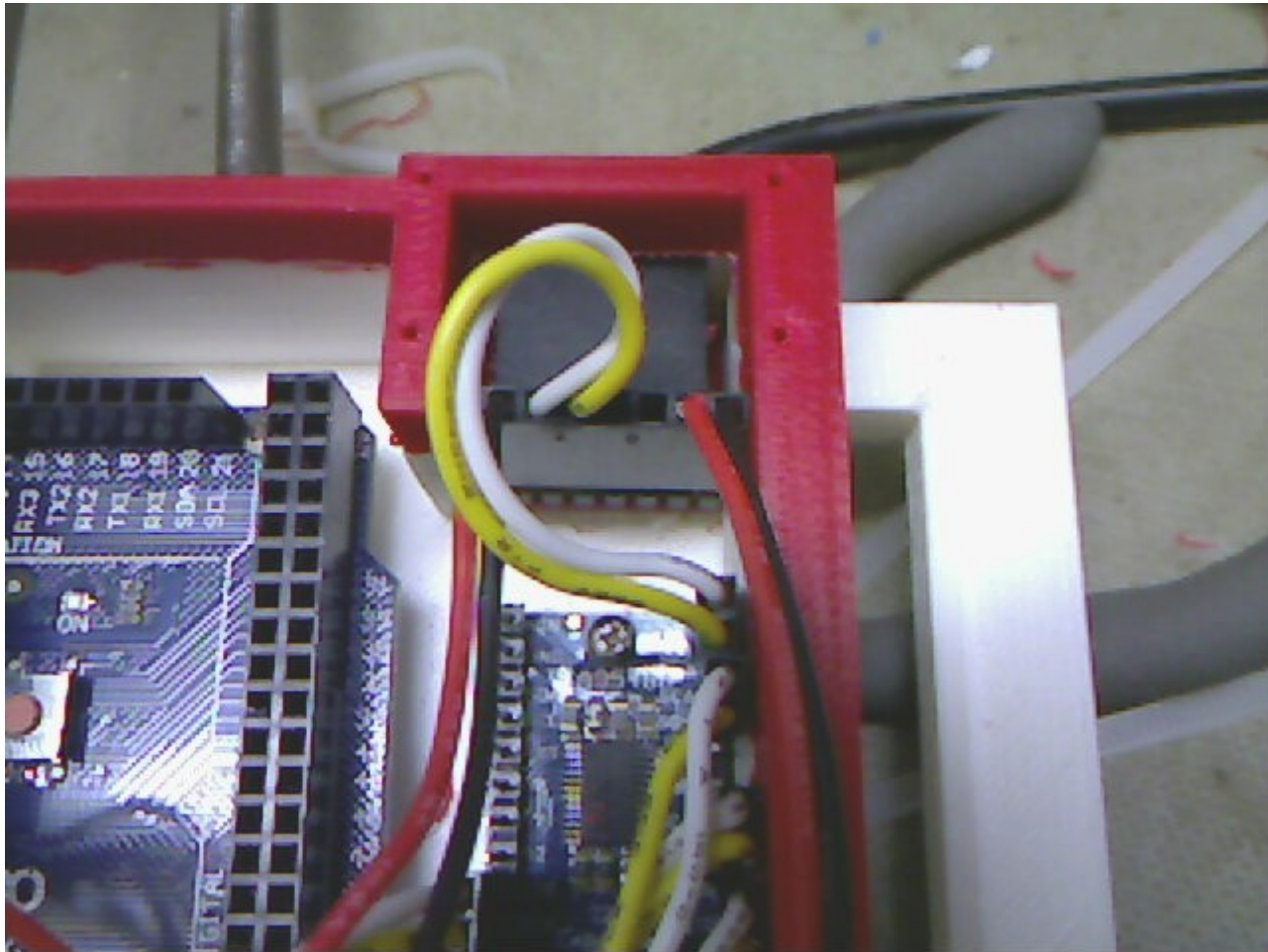
- Install two wires On the waist connector.
- Pin 3 White goes to SC7
- Pin 4 Yellow goes to SD7



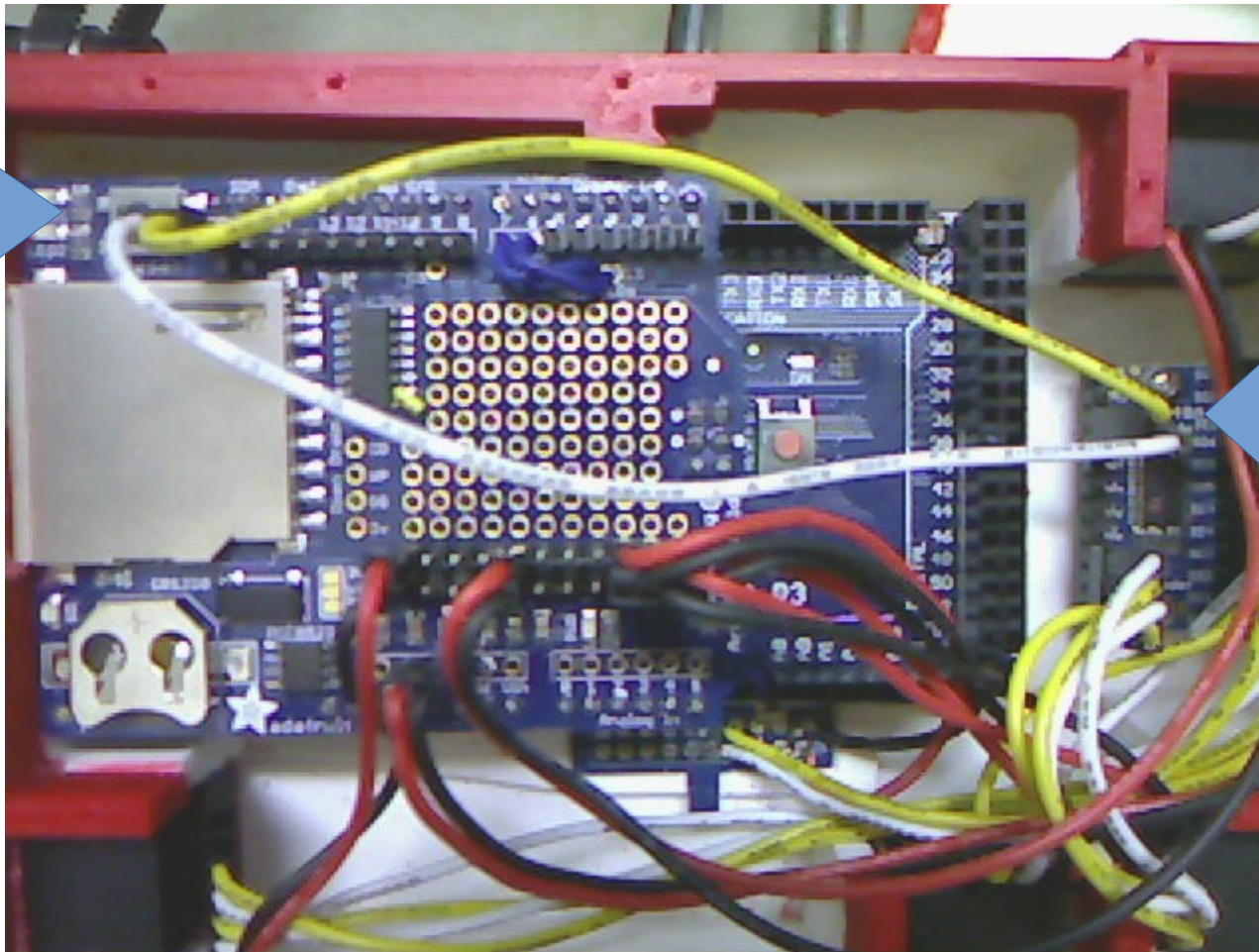
- Create a two pin to two pin harness with one white wire and one yellow wire.
- SDA – white from the Data logging shield goes to SDA white on the I2c Multiplexer.
- SCL – Yellow from the data logging shield goes to SCL yellow on the i2c multiplexer



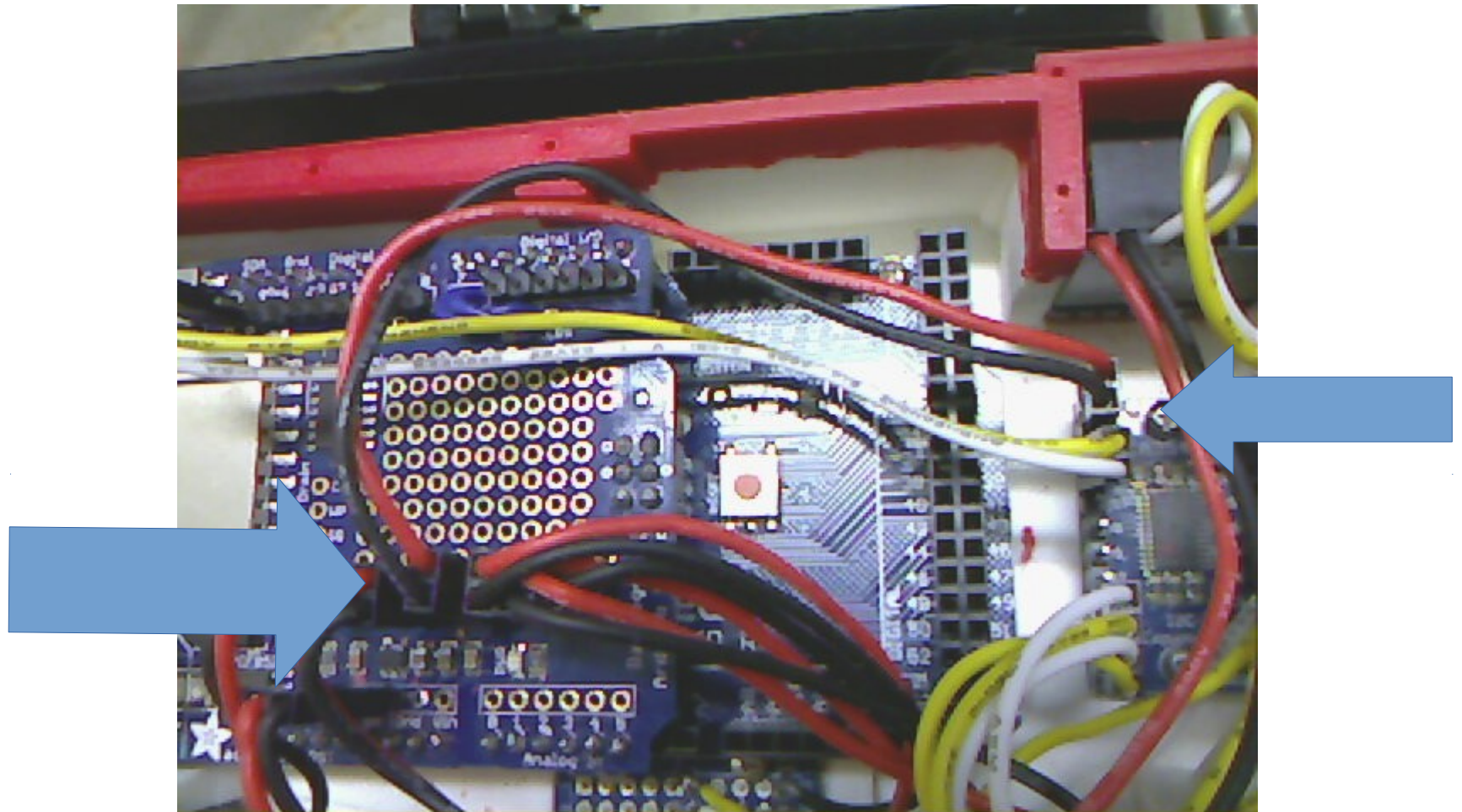
- Create a 2 pin harness to power the I2C multiplexer.
- Red Wire Vin from the I2C multiplexer goes to the 3.3V common header on the Data logging Shield.
- Black Wire Ground should go from Gnd on the I2C multiplexer to the ground common header on the Data Logging Shield.





- The LCD display in the lid has a 4 pin male header. Create four wires, with a male and female contact at each end:
- Pin 1 of LCD GND: Female contact Black wire goes to male contact marked GND on header on Mega 2560 (see below)
- Pin 2 of LCD VCC: Female contact Red Wire goes to male contact marked 5V on header on Mega2560 (see below)
- Pin 3 of LCD SDA: Female contact Yellow wire goes to pin 20 marked SDA
- Pin 4 of LCD SCL: female contact white wire goes to pin 21 marked SCL on the mega 2560. Male Contacts Pin 3 and 4 can go into a two pin housing to connect.

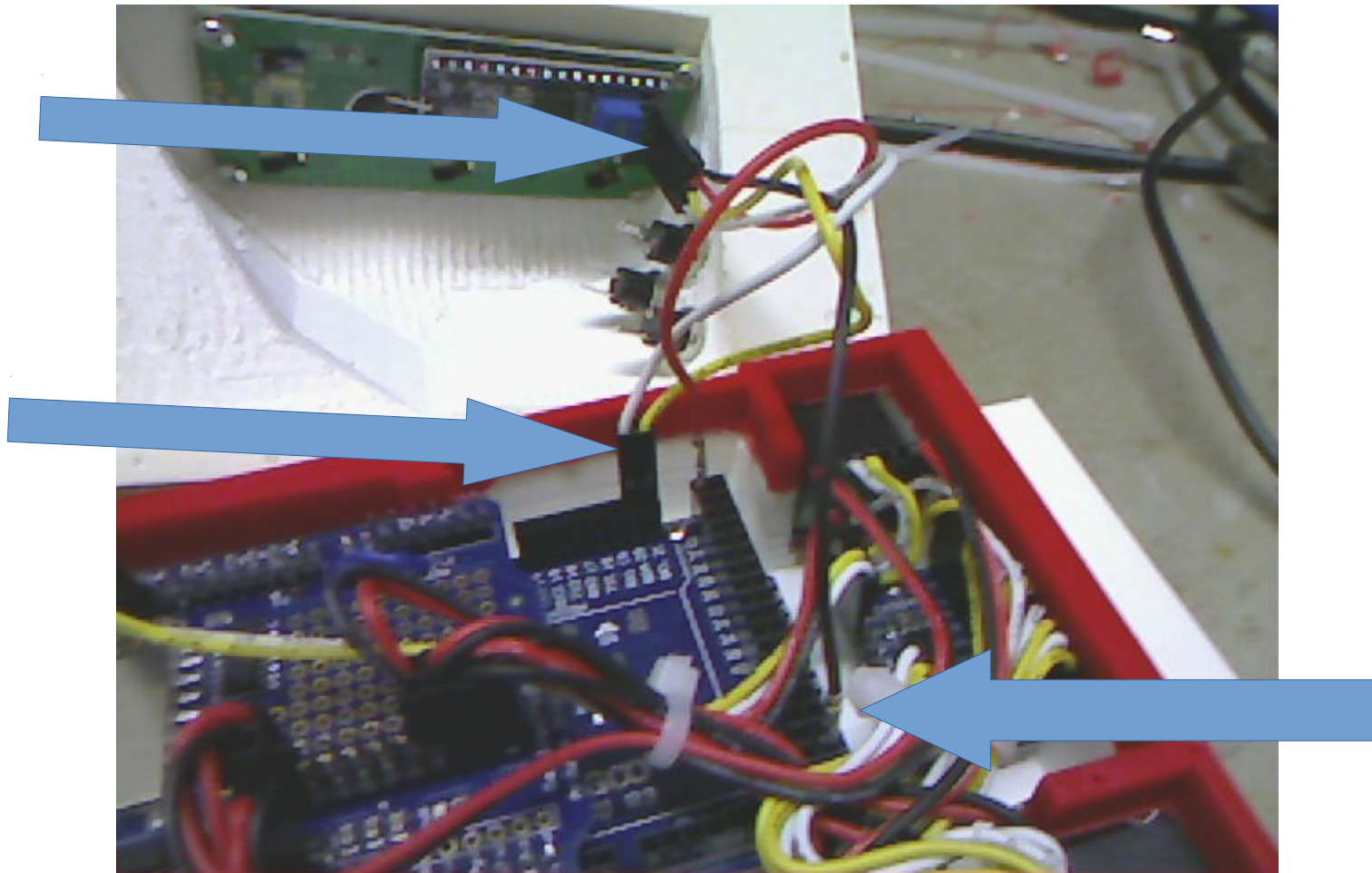

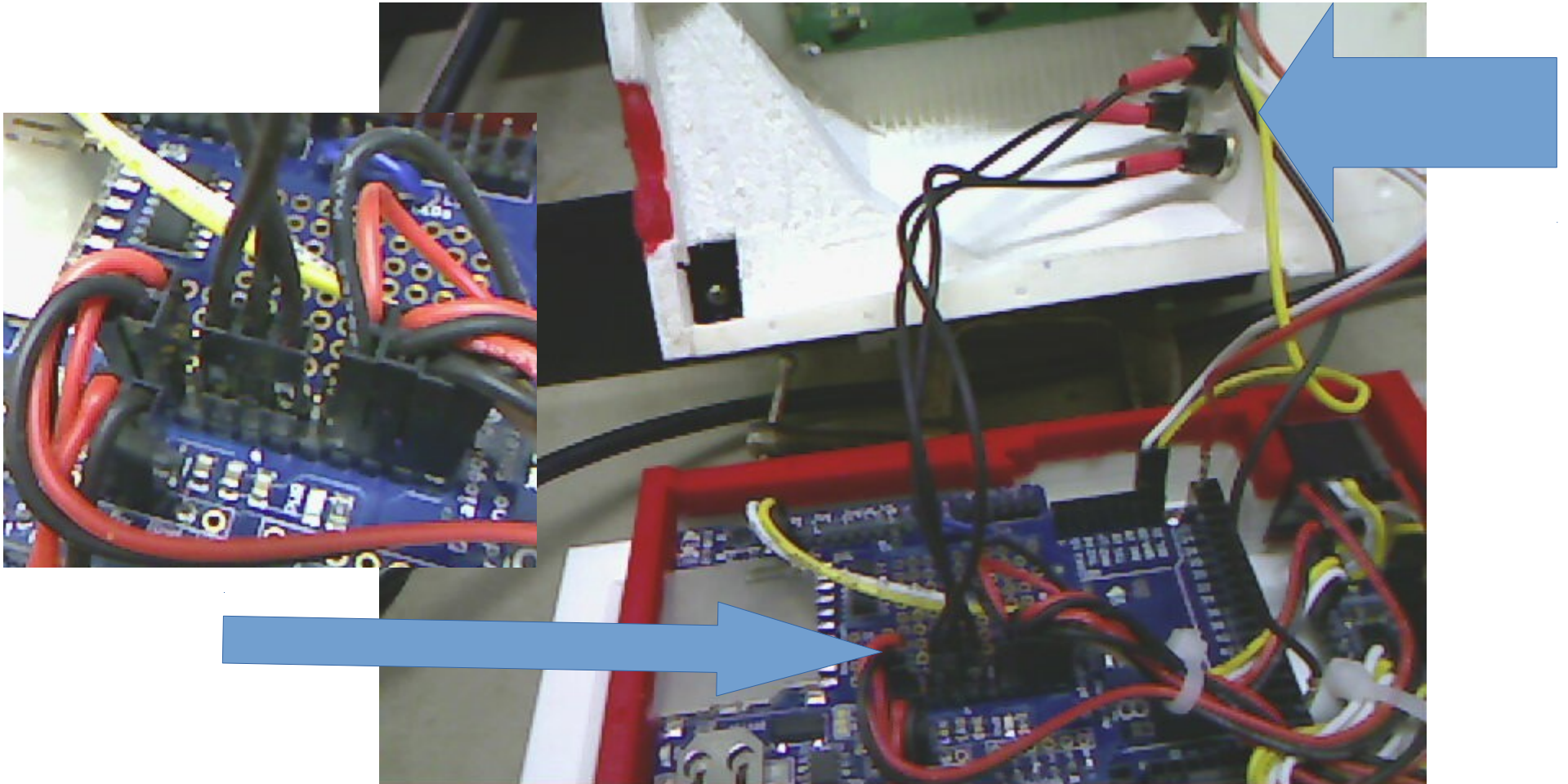- Make three black wires and solder each to a side of each of the switches. Take the other end to a 3 pin housing and connect it to the ground side of the 3.3V common power header (as shown)



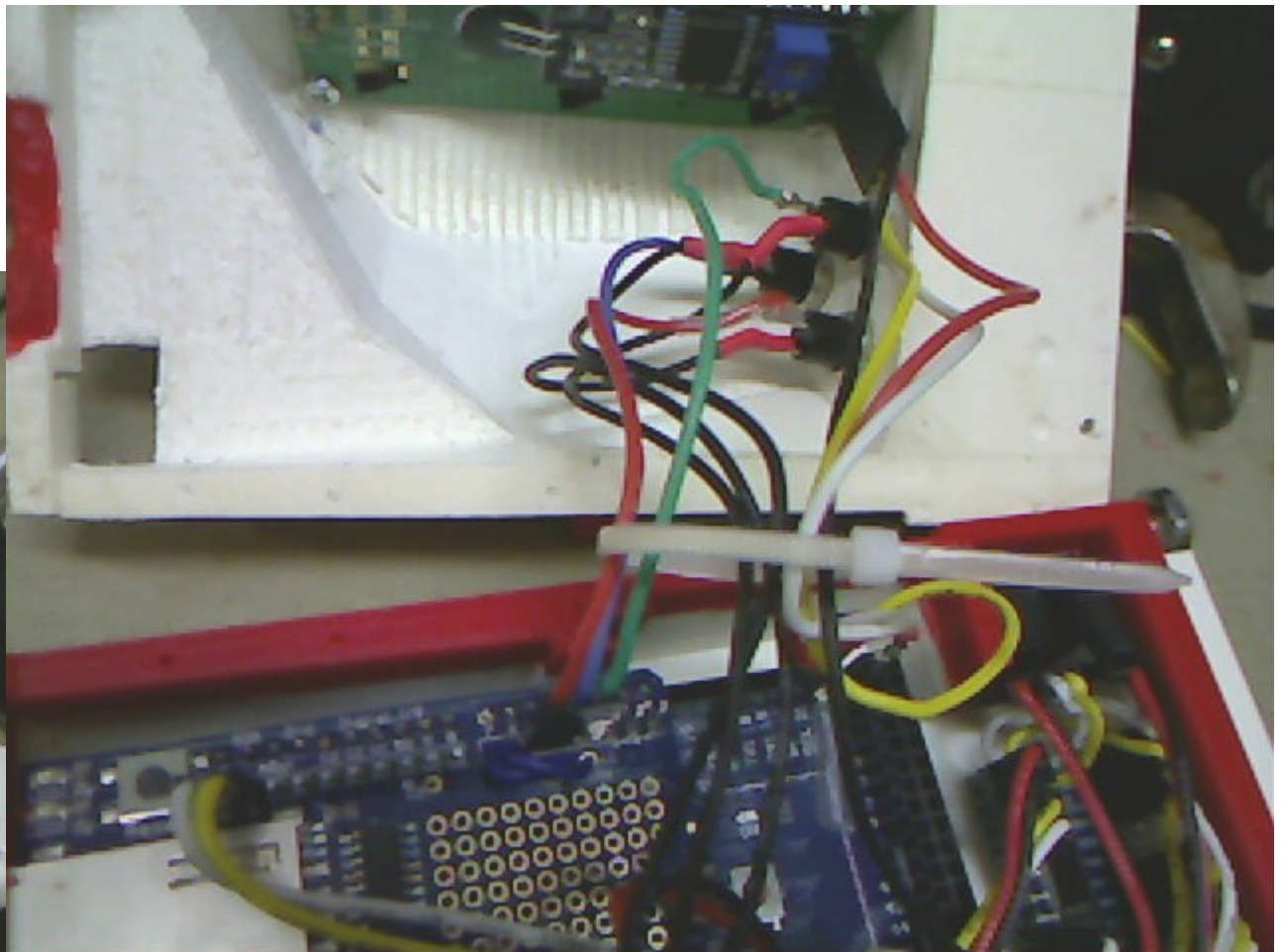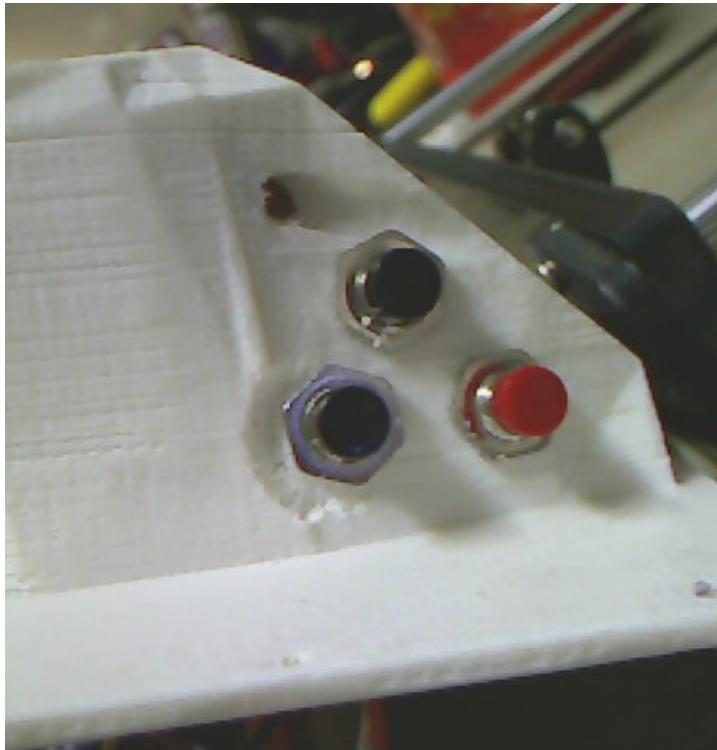- Make another 3 pin female house and connect with the following.
- Red Wire goes to red switch and goes to pin 5 on the data logging shield.
- Blue wire goes to bottom switch in photo and goes to pin 6 of the data logging shield.
- Green Wire goes to top black switch in photo and goes to Pin 7 of the data logging shield.



It's done!!!

